


- Q1. What 3 things cause signal loss in wires
- Q2. When do you start needing transmission lines
- Q3. What is a transmission line
- Q4. A 50Ω (Z_0) line is connected to an open circuit what is the reflection coefficient Γ ?
- Q5. A 50Ω line is connected to a short circuit, what is Γ ?
- Q6. A 50Ω line is connected to a matched load (50Ω) what is Γ ?
- Q7. A Sig gen with output $R=50\Omega$ is connected to a 75Ω line how much voltage is delivered onto the line if its output is $10V$

Q8. If the line in Q7 is terminated with a 50Ω load calculate the size of the first 3 reflections on the line

Q9 What voltage will the line settle to?

Q10. A sig gen with output $R = 100\Omega$ is connected to a 50Ω line with a 75Ω load connected and voltage of 12 V . Calculate the first 5 reflections & final settled voltage of the line.