

The Complete Smith Chart

Black Magic Design

Series

Example ① Single stub match. @ $Z_0 = 50 \Omega$

$$Z_L = 20 + 10j \Omega \quad (\text{ohms so impedance})$$

① Normalize value. Impedance so $\div Z_0$

$$z = 0.4 + 0.2j$$

② Plot on chart. z

③ Move away from the load along the transmission line toward the generator, clockwise round the VSWR circle

④ The first option is A on the matching circle the shortest distance along the line then B . so 0.125λ to A & 0.302λ to B

⑤ $A = 1 + j$ so $+j$ needs removing so we will add a stub with a value of $-j$

⑥ Add stub. To keep stub short we choose an open ckt. (ok)

⑦ We lengthen the stub until we hit $-1j$.

⑧ So starting at 0.25λ and rotating back the generator until $-1j$ at 0.376λ

⑨ Stub length

$$= 0.376 - 0.25$$

$$= \underline{0.126\lambda \text{ o/c}}$$

$$0.25\lambda$$

⑩ Option 2 for

$$B = 1 - j$$


we need to add $+j$ to get to a match.


⑪ Choose s/c stub and lengthen until it equals $+j$

⑫ So from 0λ


$$\text{to } 0.126\lambda$$
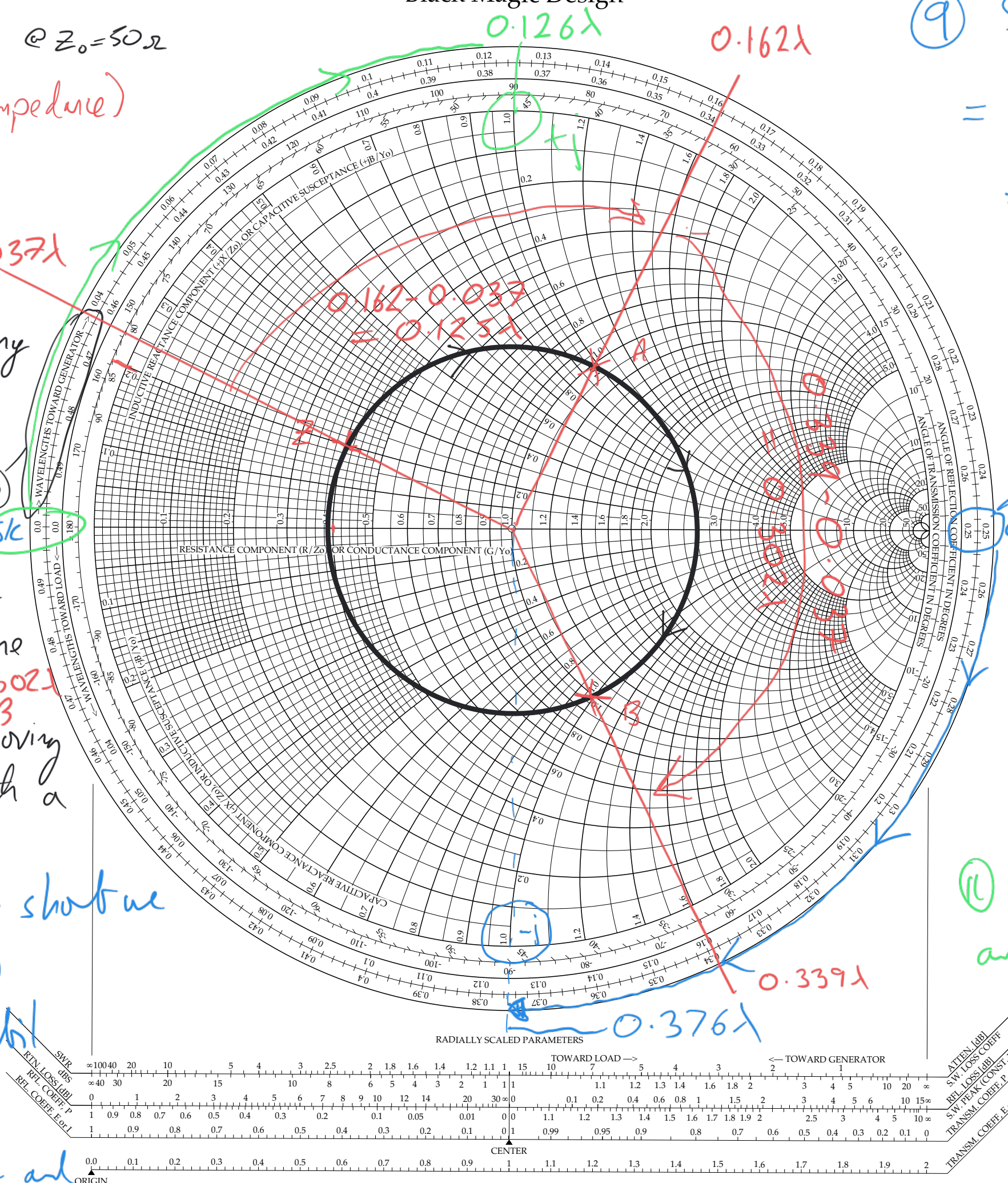
$$\text{stub length} = \underline{\underline{0.126\lambda \text{ s/c}}}$$



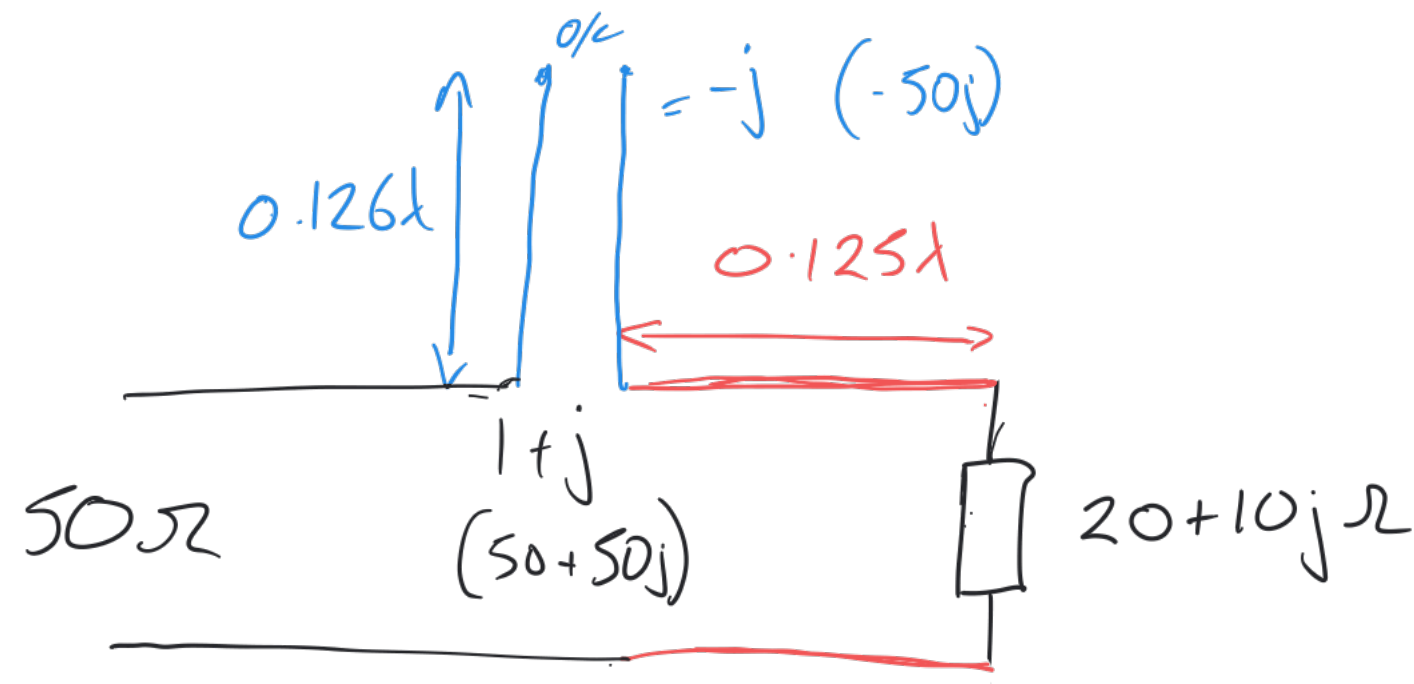

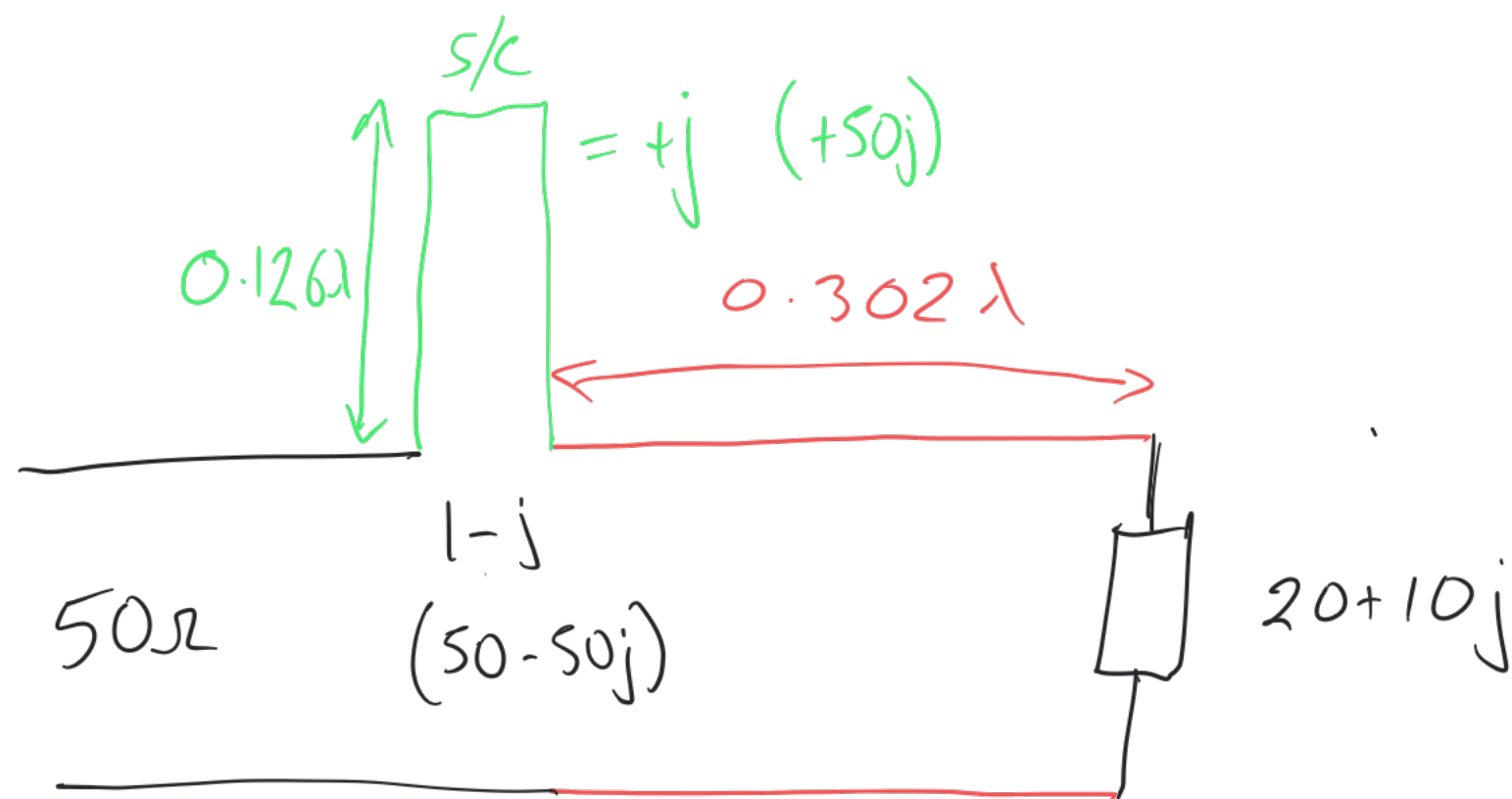A. Rotate 0.125λ towards gen to hit matching circle at $1 + j$. Add o/c stub of length 0.126λ giving value of $-j$.



B. Rotate 0.302λ onto matching circle at $1 - j$. Add short ckt stub of length 0.126λ to give value of $+j$

The Complete Smith Chart

Black Magic Design

Parallel single stub.

$$Z_L = 100 - 100j \, \Omega$$

$$(\div 50) \Rightarrow 2-2j$$

Plot Z . Transpose to Y
and admittance - parallel.

Through curve same
dis bore other side.

$$y = 0.26 + 0.24j$$

Rotate onto
mabding circle
towards ger.

From $0.04 \rightarrow 0.18$


$$A = 0.14\lambda$$

$$e \quad 0.04 \rightarrow 0.322$$

$$B = 0.282 \lambda$$

$$A = 1 + 1.6j$$

$$B = 1 - 1.6j$$

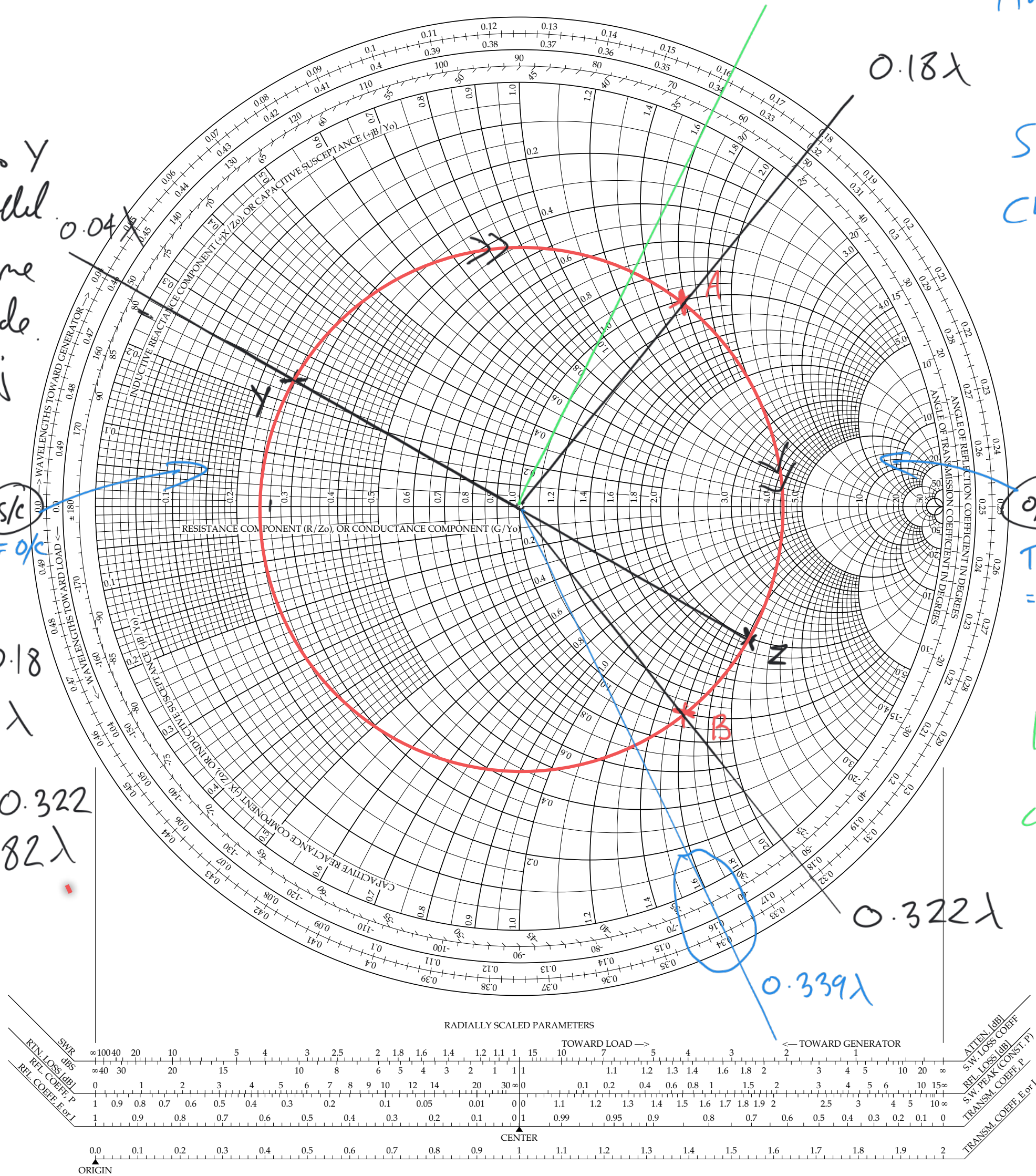

Add stubs to cancel
+ 1.6j at A.

So stat. mess = $-1.6j$

Choose s/c length

$$= 0.339 - 0.25$$
$$= \underline{\underline{0.0891}}$$



o/c

Transpoen
= S/C

Add stats to add
1-6j if option B is
chosen.


Choose o/c length

0.1611

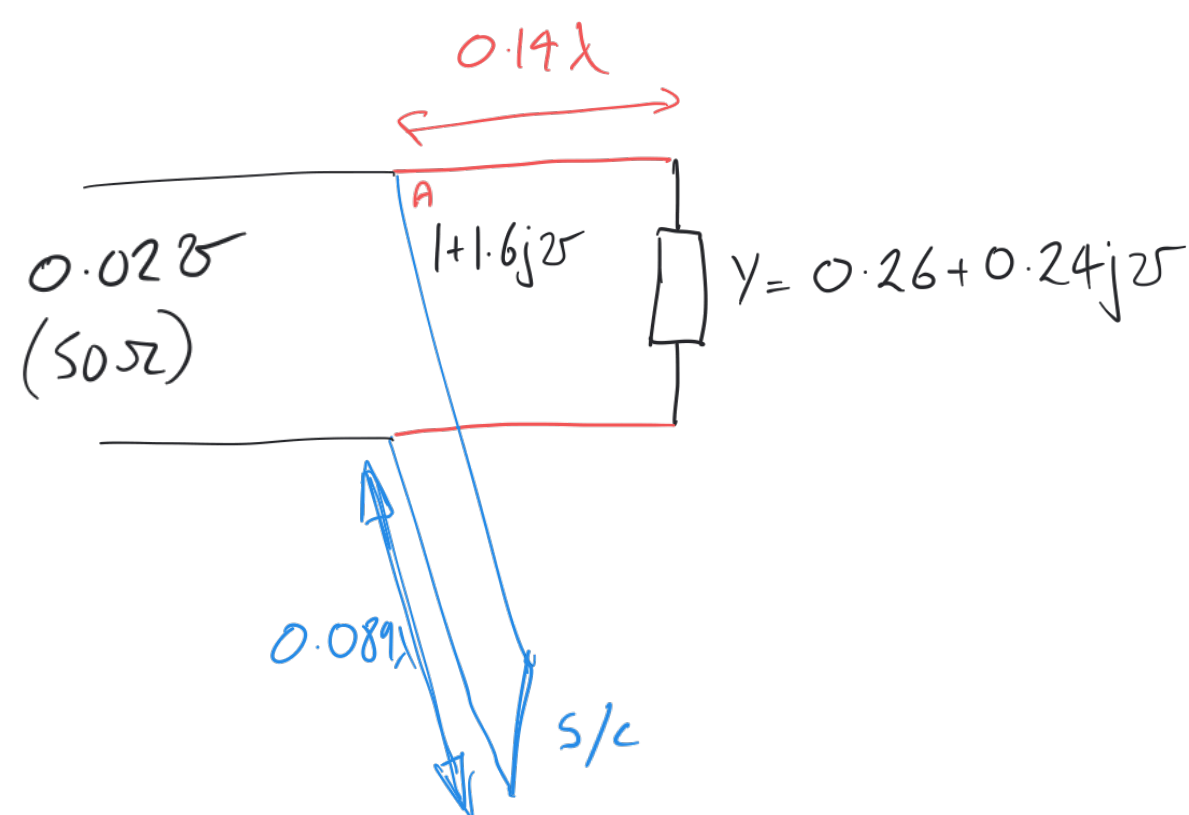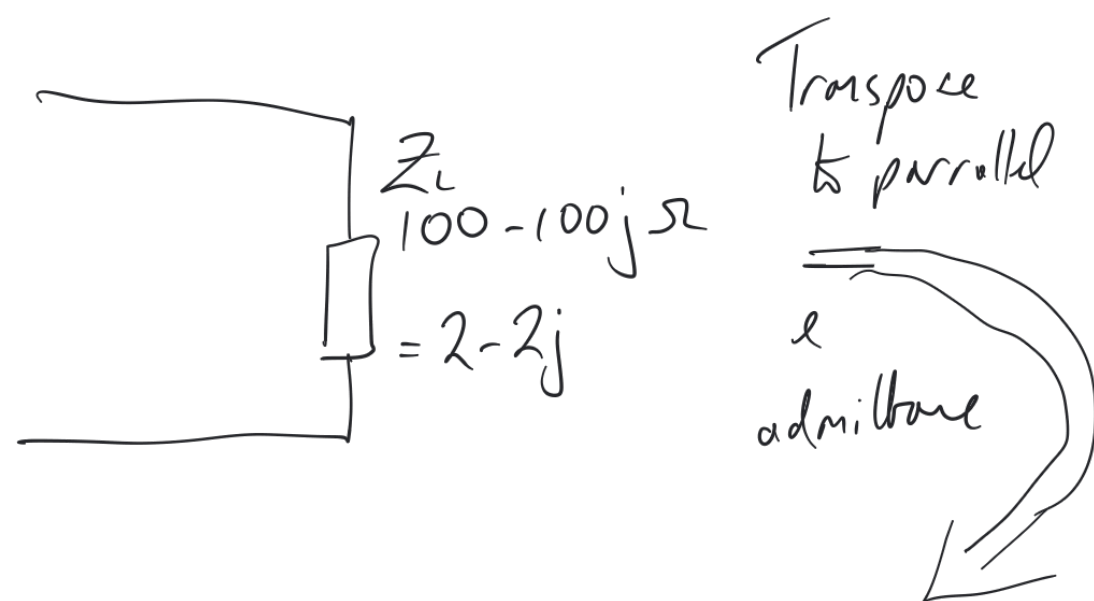

Transpose your impedance to parallel
 and an admittance.
 You would not need to do this if you
 were given an admittance to start with.
 Transpose the o/c & s/c points to admittance.

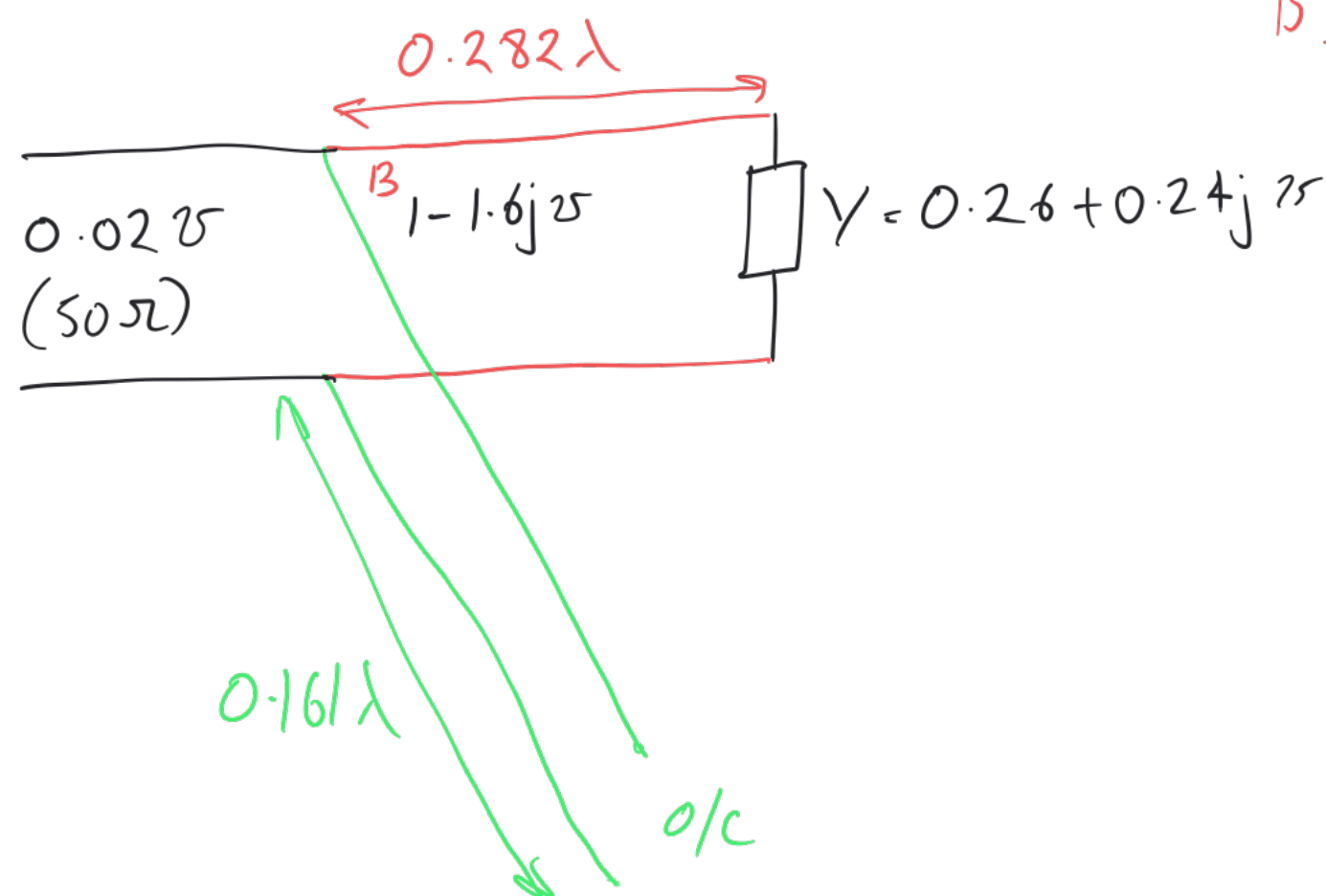A. Rotate Y 0.14λ onto matching circle
 Add stubs to cancel $+1.6j$
 In this case a s/c stub of length 0.089λ
 $= -1.6j$




B. Or.. rotate Y 0.282λ onto pt B on matching
 circle.

Add stubs to cancel $-1.6j$
 In this case an o/c stub, length $0.161 \lambda = +1.6j$


The Complete Smith Chart

Black Magic Design

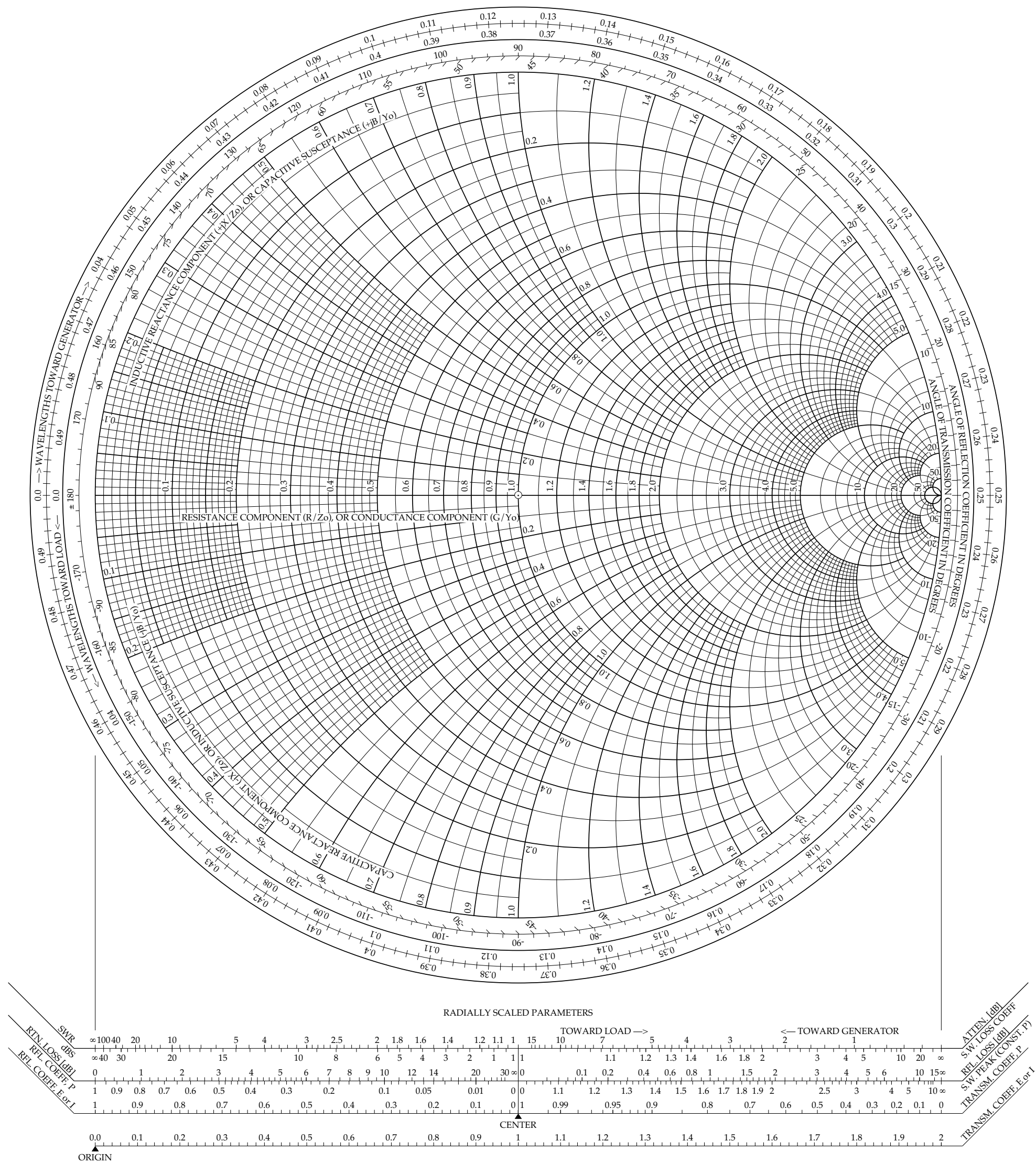


The Complete Smith Chart

Black Magic Design

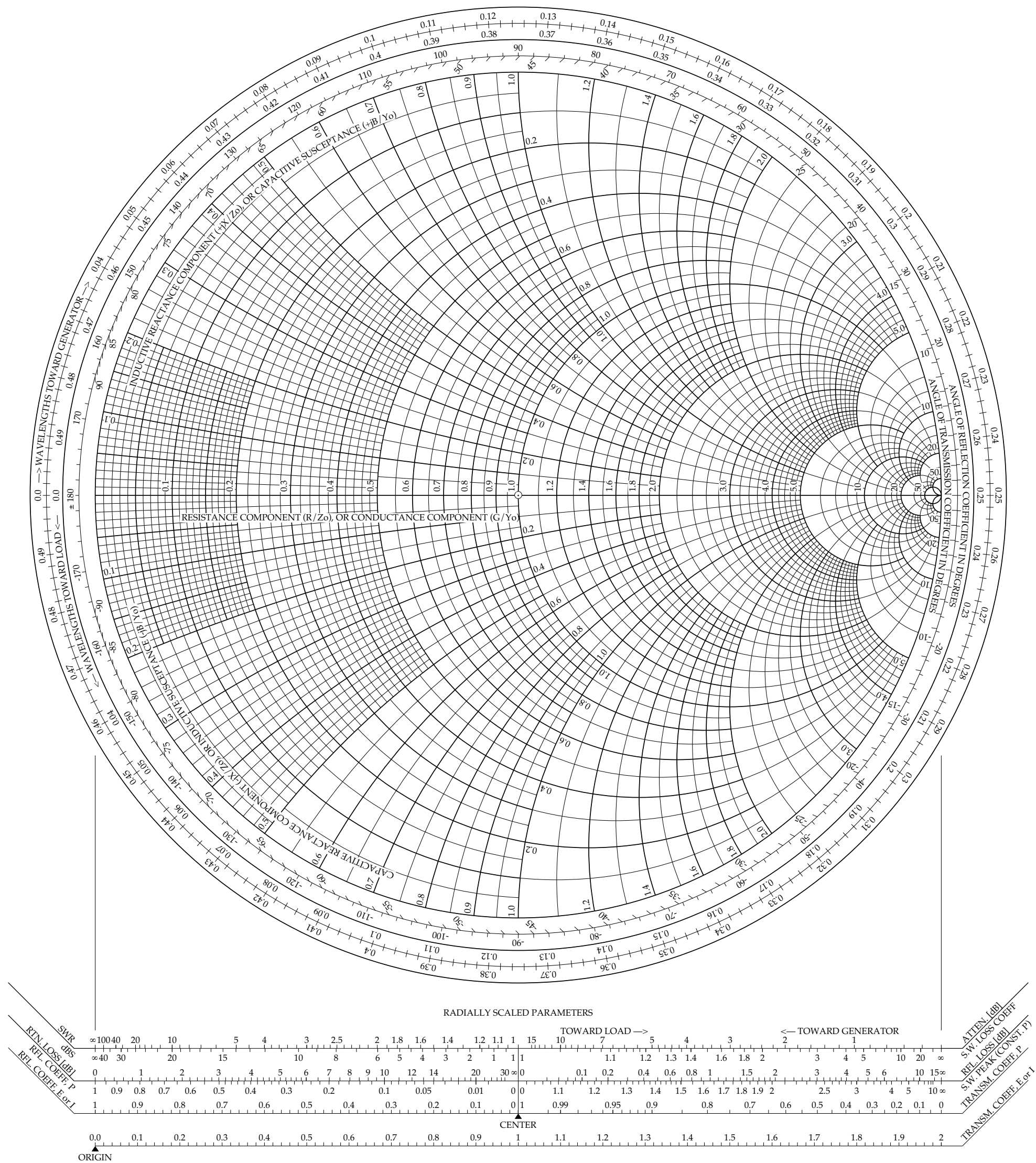


The Complete Smith Chart

Black Magic Design

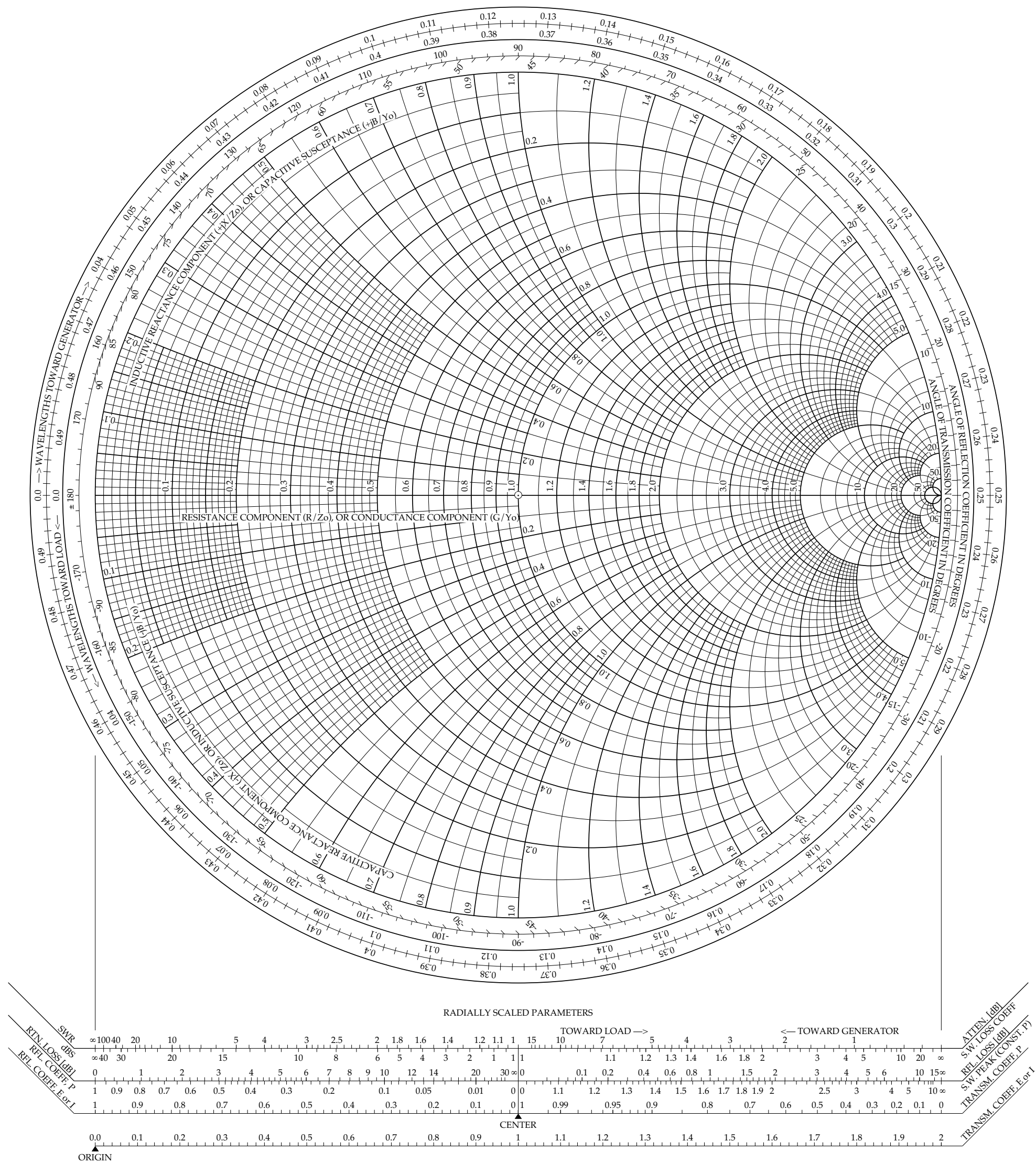


The Complete Smith Chart

Black Magic Design

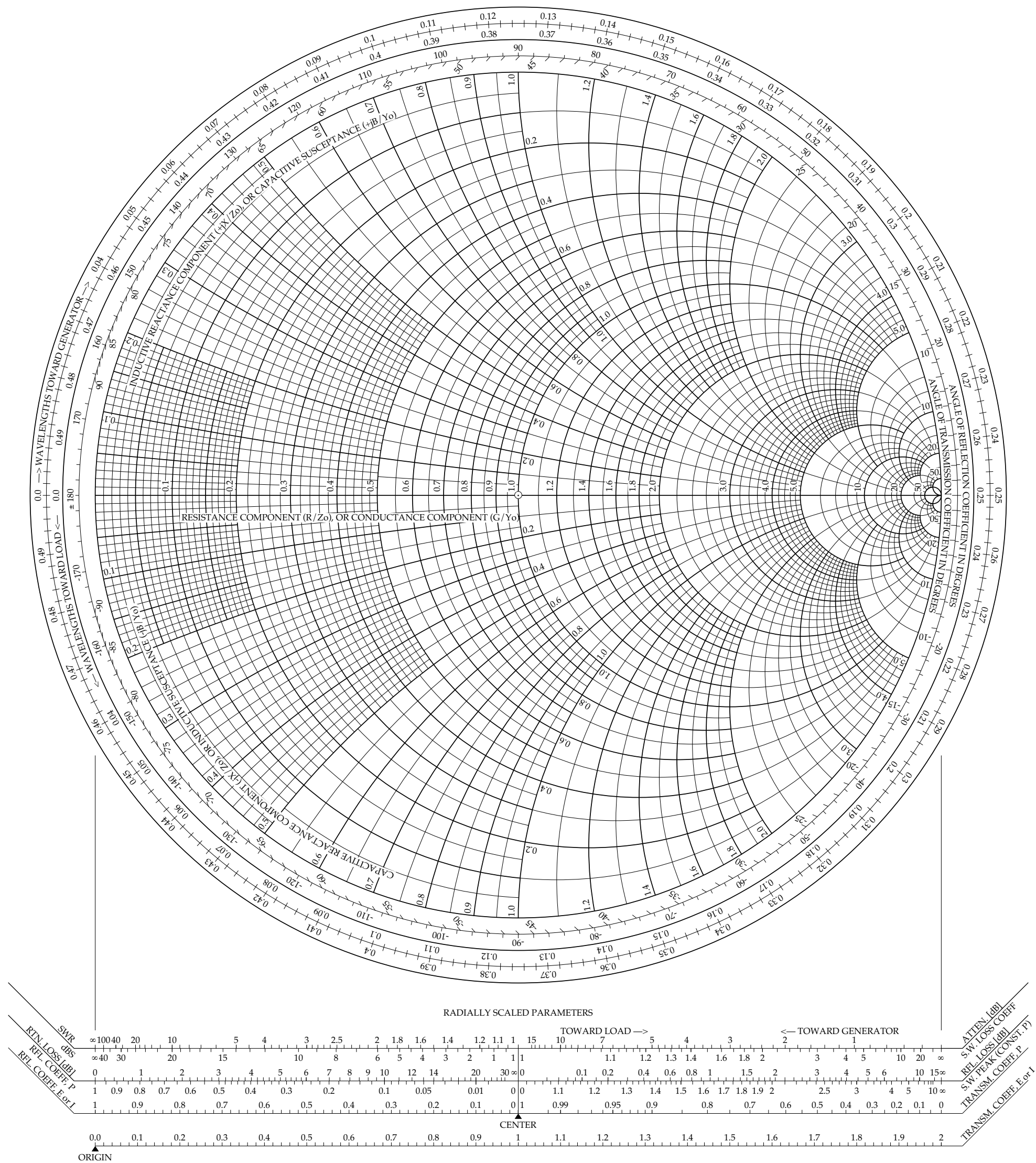


The Complete Smith Chart

Black Magic Design

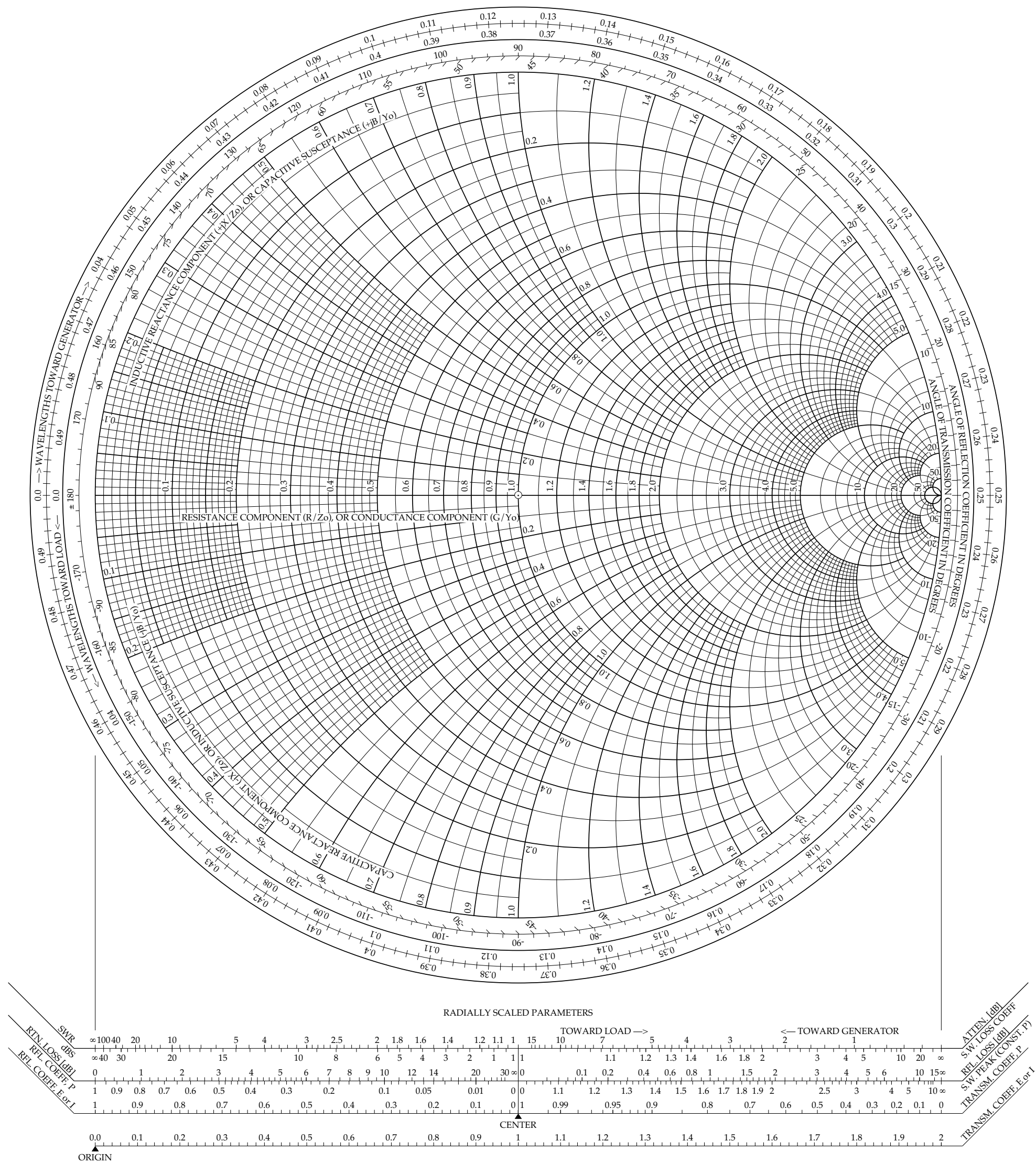


The Complete Smith Chart

Black Magic Design

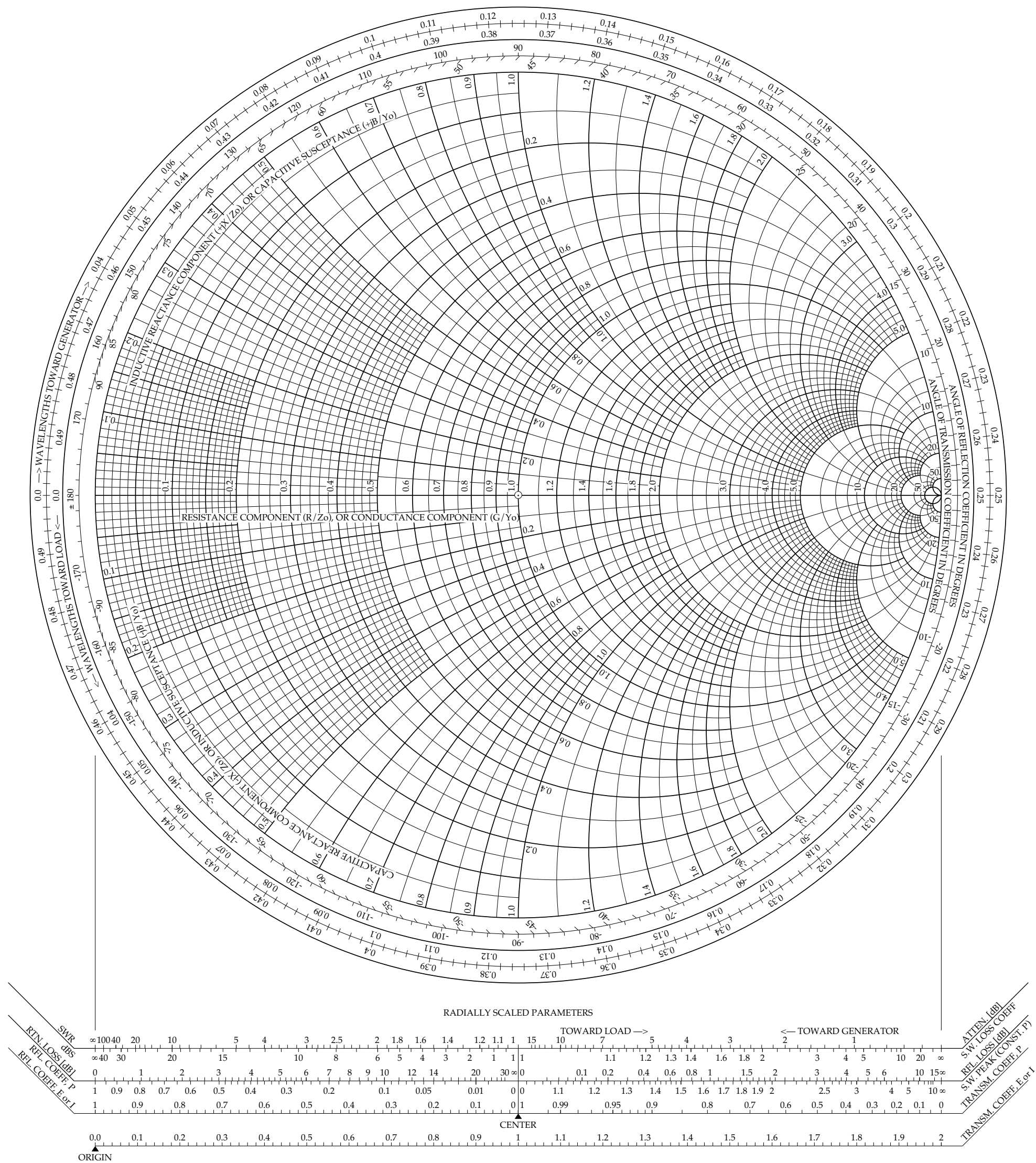

The Complete Smith Chart

Black Magic Design

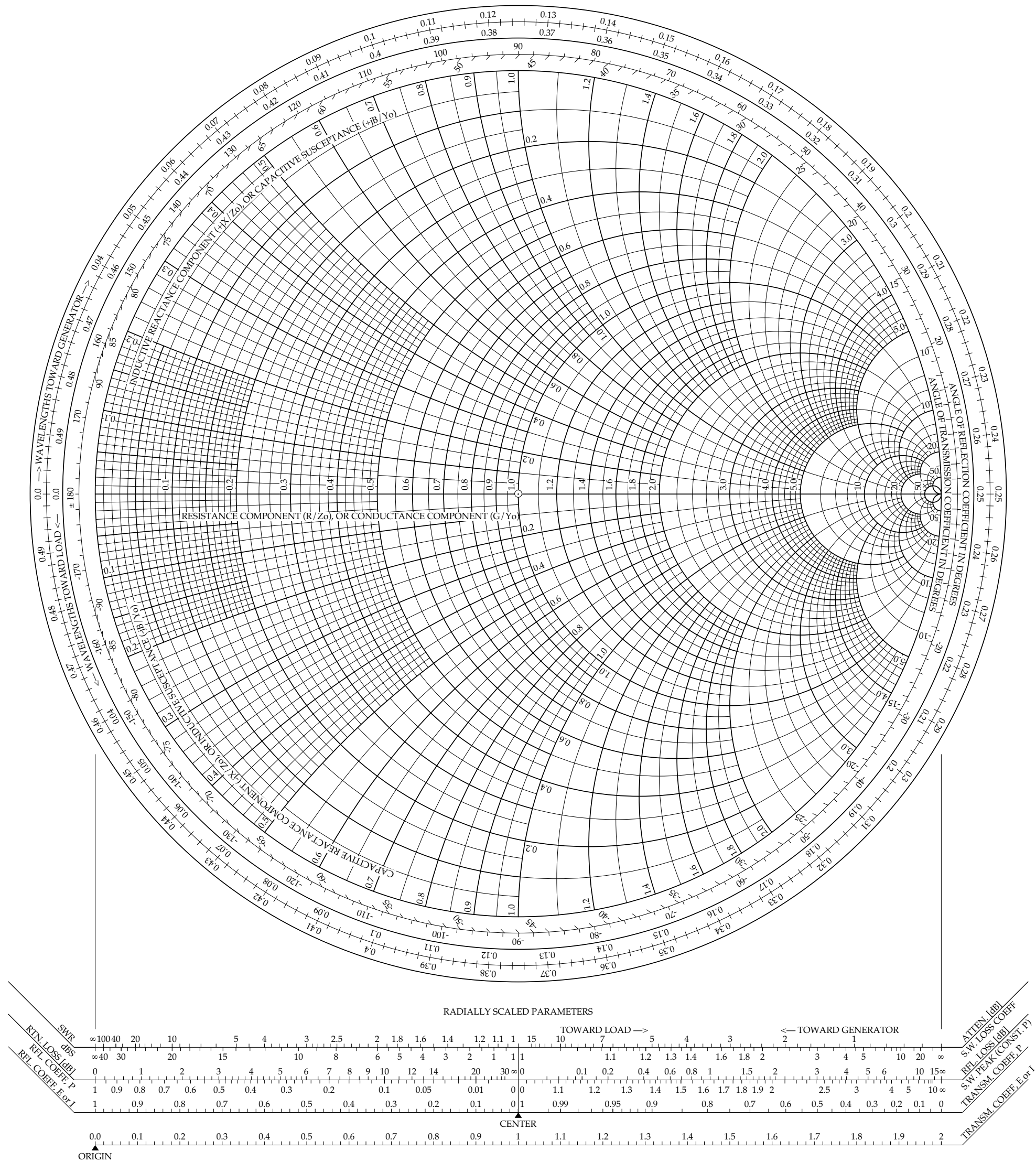

The Complete Smith Chart

Black Magic Design

