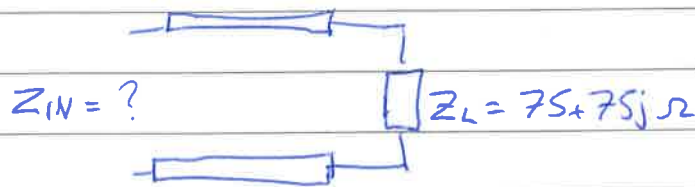


## Stub Match & Smith Chart Questions

1. RF system. What will be its characteristic impedance  $Z_0$ ?
2. In this RF system the normalized value of  $75 + 75j \Omega$  will be what?
3. Plot this on the Smith chart.
4. Using the Smith chart find:
  - i) Reflection coefficient
  - ii) VSWR as a value and in dB.
5. The  $75 + 75j \Omega$  load is on a  $0.12\lambda$  bit of coaxial cable. What impedance would you see at the end of the cable? ( $Z_{in}$ )



6. What is the VSWR at  $Z_{in}$ ?
7. Where on the coaxial cable would you add a series stub? (2 options)
8. What type of stub & how long (shortest possible).  
(Find all combinations for practice)