

Electrical and Electronics Engineering and Robotics

ELEC345 High Speed Communications
Conductors at RF and Transmission Lines

Dr Toby Whitley



UNIVERSITY OF
PLYMOUTH



High Speed Communications

Wired and Wireless

- 10-11 lectures / tutorials in Fitzroy 107 9am
- Tutorials on alternate weeks, Smeaton 307 11am
- 11 labs in Smeaton 307 2pm
- Exam
 - 70% of Module mark
 - 5 Questions, answer four
- Coursework
 - 30% of Module mark
 - A design exercise alongside several benchmark tests
 - Presented in week 12 along with a technical note summarising the work.
- Staff
 - Dr Toby Whitley. Reynolds 114
 - John Welsh. Technical office and Smeaton 307



UNIVERSITY OF
PLYMOUTH

Topics, not in order

- Conductors at RF and Transmission lines
- dBs and link budgets
- Antenna
- Cellular systems and channel access
- L Matching and Smith Charts
- The Wireless environment
- Diversity Techniques and diversity combination
- Wi-Fi
- MIMO
- Stub matching
- RF Filters



UNIVERSITY OF
PLYMOUTH

What are transmission lines?

- The following slides and lectures give an introduction to their basic theory, behaviour and properties.
- Why are they important?
 - A means of transmitting energy with reduced loss over a conductor
 - A way of maintaining the integrity of data and signals
- When does a wire become a transmission line?
 - Frequency, wavelength, power, length, diameter??
- What are their practical applications and limitations?
 - Connecting our modern world and its devices.
- Examples of common transmission lines will be given



UNIVERSITY OF
PLYMOUTH

Why are they needed?

- Wires at DC
 - Resistance is set by:
 - Material
 - Dimensions
 - $\text{Resistance} = \text{Length} / (\text{Conductivity} * \text{Cross Sectional Area(CSA)})$
 - $\text{Resistance} = \text{Length} * \text{Resistivity} / \text{CSA}$
 - At DC the whole conductor is used to carry the current. Double the CSA half the resistance (ohms law)
- AC resistance
 - Increases with frequency
 - Why?




Skin Effect

- AC and more so at RF frequencies
 - Inductance
 - Increases with frequency
 - $X_L = j\omega L$ where $\omega = 2\pi f$ so $X_L = j 2\pi f L$
 - Caused by magnetic flux and the density of the field line through the conductor.
 - As frequency increases so does the density of the magnetic flux lines in the conductor (induced inductance).
 - This increases the AC resistance but not in a uniform way.
 - The result is the RF current flow migrating to the outer edges of the conductor to flow along the path of least resistance.



Skin effect

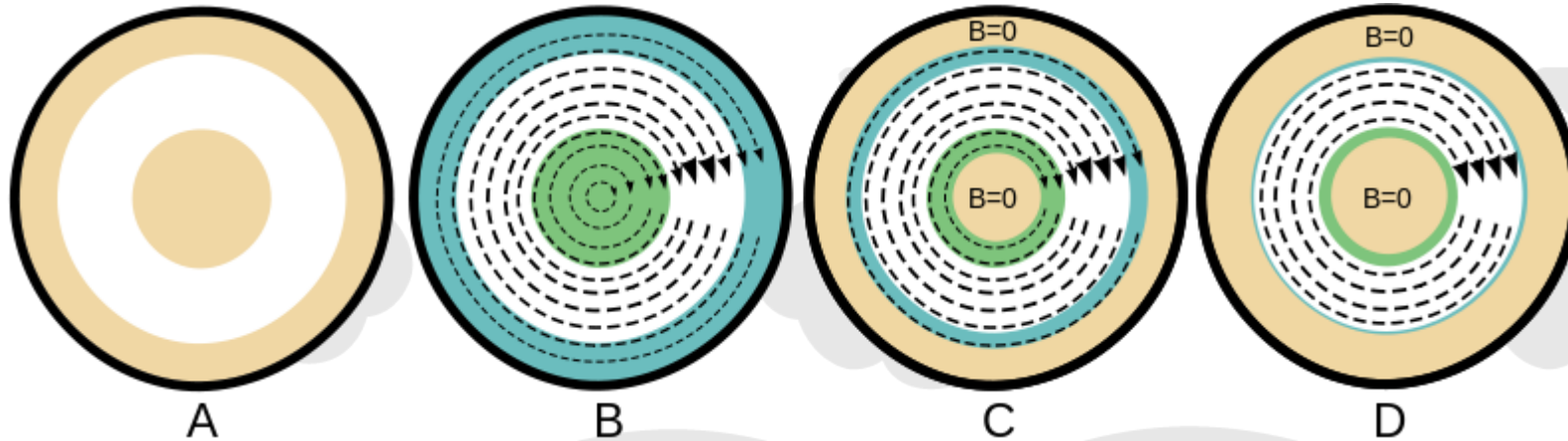

A: No current flow

B: Low frequency current flow


C: Medium Frequency

D: High Frequency



UNIVERSITY OF
PLYMOUTH

Skin effect

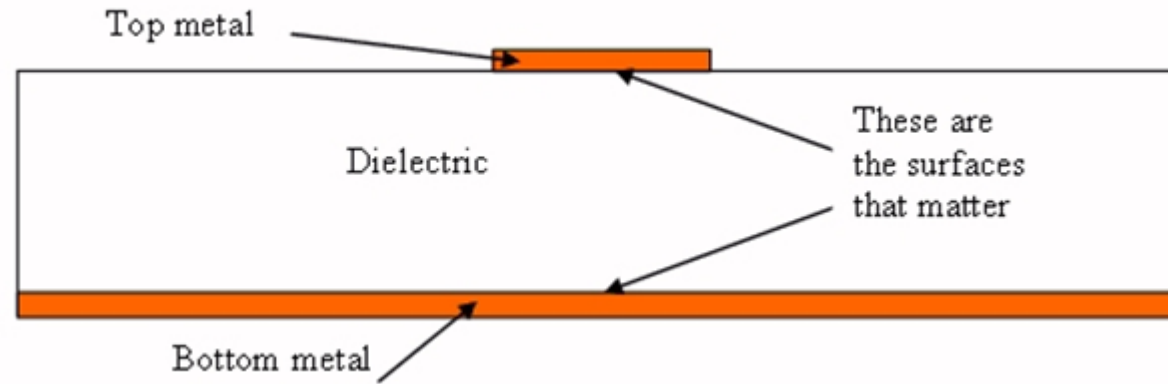

Where will the currents be flowing?

High frequency in micro strip. Take note of the field diagram of this later in the slides.



UNIVERSITY OF
PLYMOUTH

Skin Depth

- These skin effects lead to a reduction in the effective RF cross section of the conductor.
- Skin depth is defined as the depth at which the current density has fallen by 1/e or 37% of its surface value.

- **Skin Depth Formula**

$$\delta_s = \sqrt{\left(\frac{1}{\pi f \mu \sigma}\right)} = \sqrt{\frac{2}{\omega \mu \sigma}} = \sqrt{\frac{\rho}{\pi f \mu}}$$

$$\omega = 2\pi f$$

- Where f is the operating frequency (Hz)
- μ is the permeability of the conductor (H/m)
 - $\mu = \mu_r \mu_0$ (μ_r is usually 1 and $\mu_0 = 4\pi \cdot 10^{-7}$)
- σ is the conductivity of the conductor (S/m)
- ρ is resistivity ($\Omega \cdot m$)
 - » Dependant on only three things
 - (Bulk resistivity is a measure of how resistive a material is. It is the reciprocal of bulk conductivity.)



$$\delta_{\text{Gold}} = \sqrt{\frac{2.44 \times 10^{-8}}{\pi \times 1 \times 10^6 \times 4\pi \times 10^{-7}}} =$$

Calculations

- Skin depths of common materials at various frequencies:

ρ ($\mu\Omega/\text{cm}$) ($\Omega \cdot 10^{-8}/\text{m}$)	Material	Frequency	Skin depth (μm)
1.673	Copper	1MHz	66
	Copper	500MHz	2.9
	Copper		
1.59	Silver	1MHz	64
	Silver	500MHz	2.8
	Silver		
2.44	Gold	1MHz	
	Gold	500MHz	
	Gold		


Q? What would be the skin depth of the perfect conductor?

$$\mu = \mu_r \mu_0 \quad (\mu_r \text{ is usually } 1 \text{ and } \mu_0 = 4\pi \cdot 10^{-7})$$

$$\delta_s = \sqrt{\left(\frac{1}{\pi f \mu \sigma}\right)} = \sqrt{\frac{2}{\omega \mu \sigma}} = \sqrt{\frac{\rho}{\pi f \mu}}$$



Skin Depth, implications

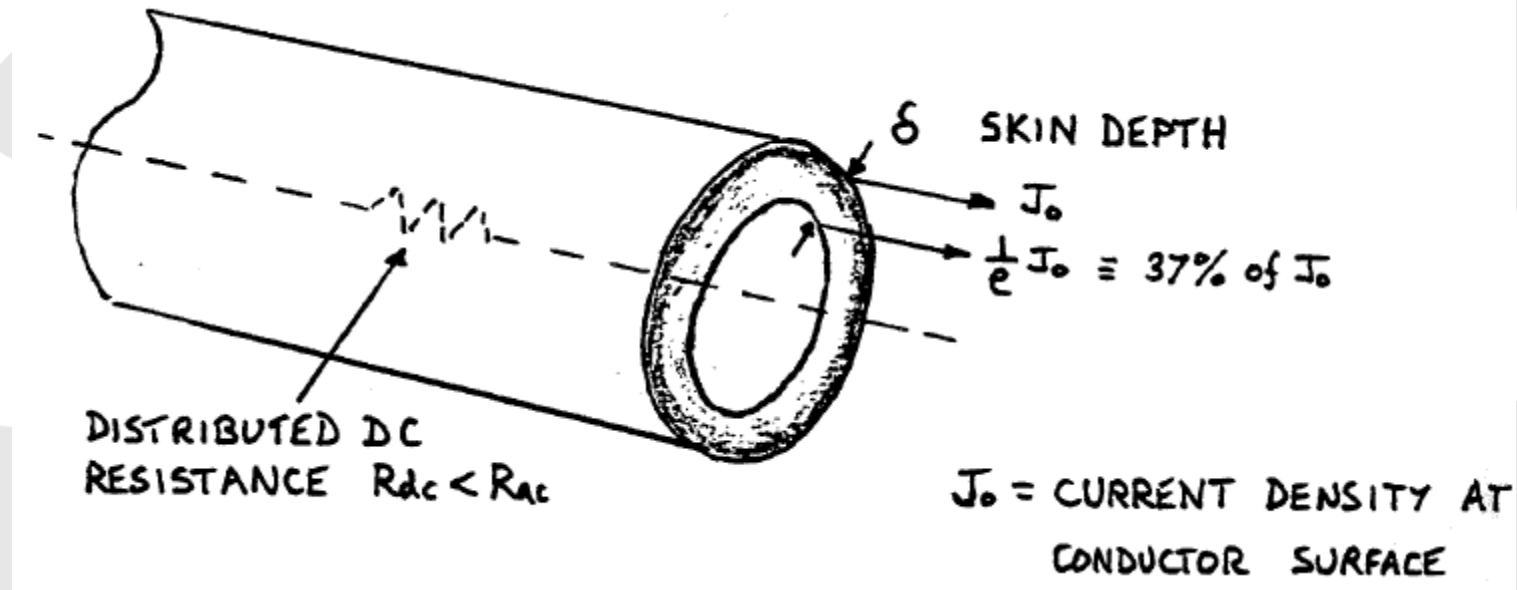

Skin Depth, implications


LITZ



TAPE



TUBE

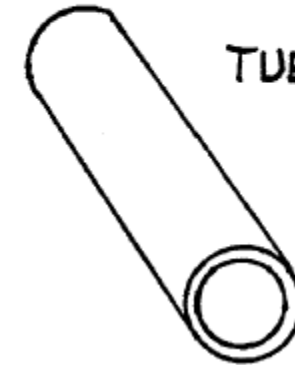

How thick do things need to be?
What implications does this have in terms of design and
Construction?



UNIVERSITY OF
PLYMOUTH

Self inductance of conductors

- It is clear from looking at skin depth effect and what we know of transmission line properties and models that conductors have distributed inductance associated with them.
- The self inductance of connecting wire is approximately **1nH/mm** which is useful to know.
- A better estimate for a circular section conductor may be obtained using the following expression:


$$L = 0.02l \left[2.3 \log \left(\frac{4l}{d} - 0.75 \right) \right] [\mu H]$$

- **Question:** If the 1nH/mm is accurate what is the diameter of the connecting wire? If the wire diameter is increased to 3mm what effect does this have?
- **Where l = wire length in cm, d = diameter of wire in cm, L = self inductance**




Lumped components : Resistors


Wire Wound Resistors

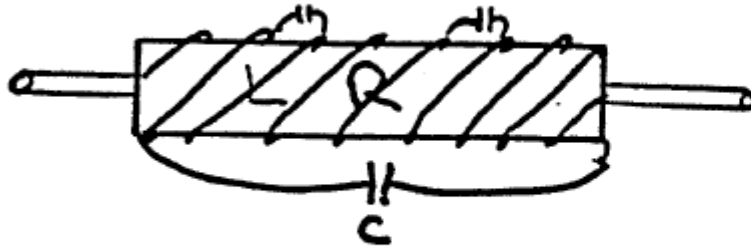

EQUIVALENT CIRCUIT


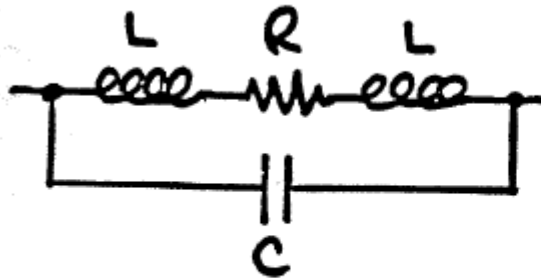


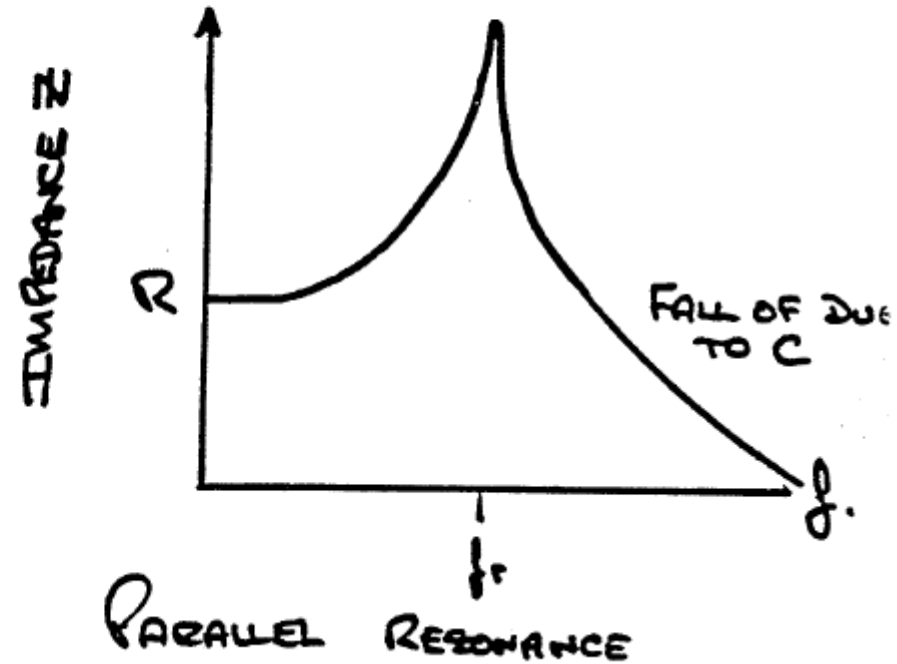- HIGHLY INDUCTIVE $\propto R$
- COIL INDUCTANCE SWAMPS LEAD INDUCTANCE




Resistors

Carbon Composition

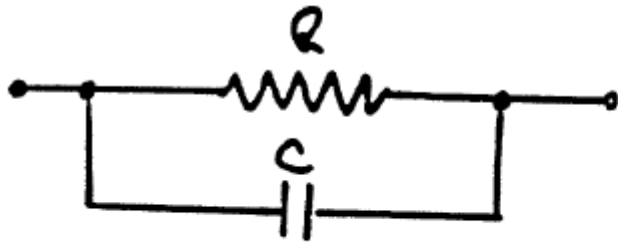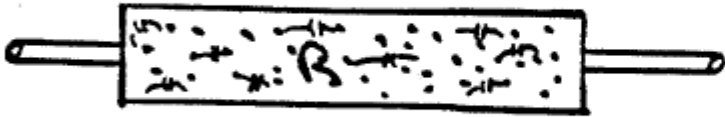


Power supplies etc.
Expensive

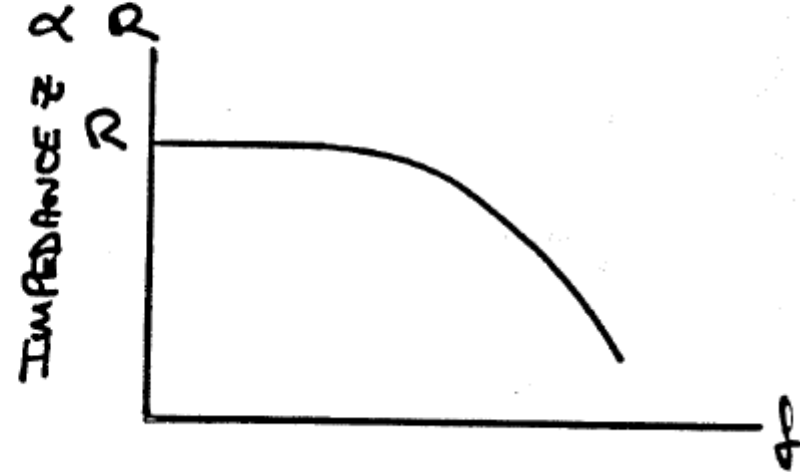- MUCH REDUCED INDUCTANCE
- HIGH INTERNAL CAPACITANCE





Resistors

High VALUE

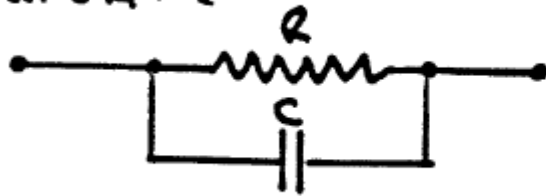

Low VALUE

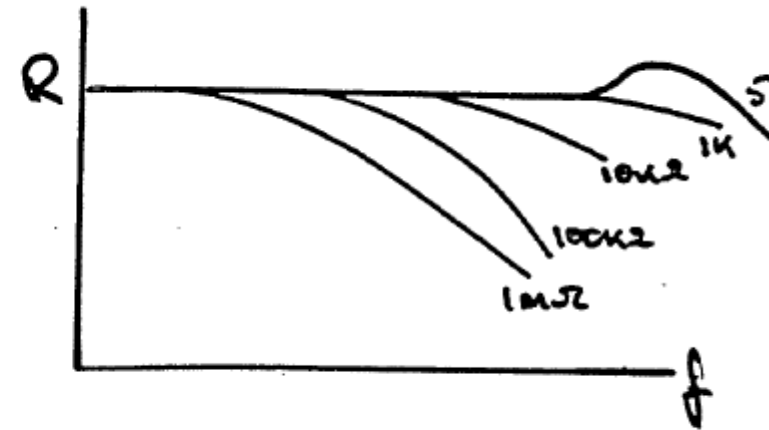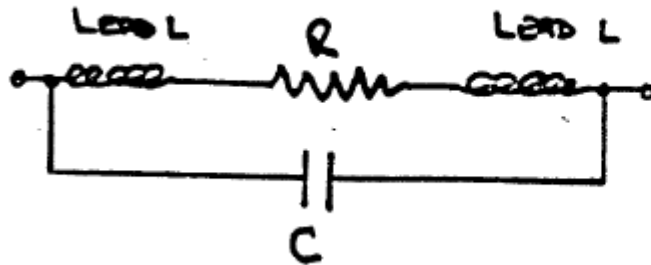


RF and microwave applications



UNIVERSITY OF
PLYMOUTH

What does make a transmission line?



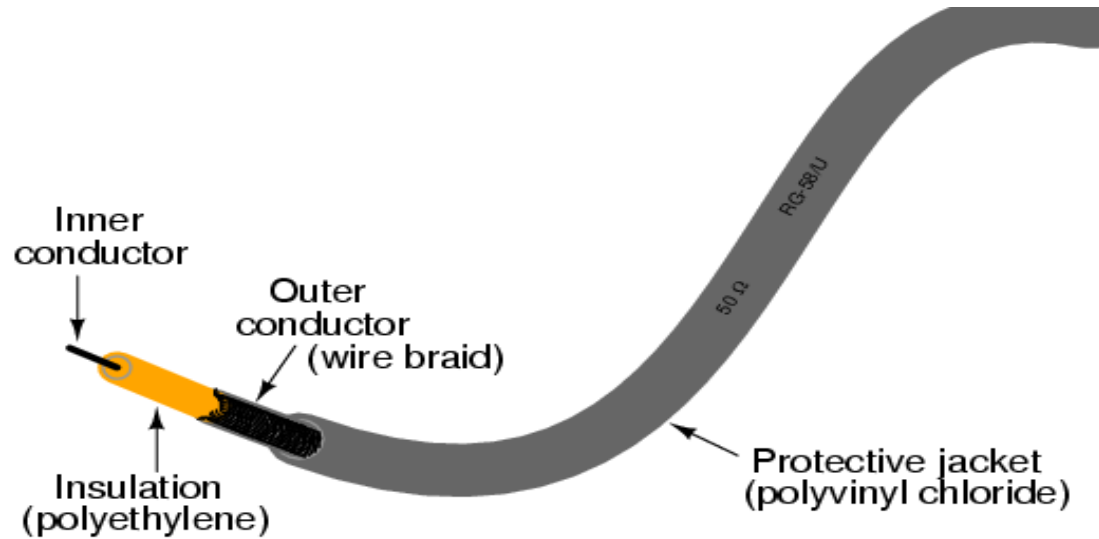


- Physical properties:
 - Two (parallel) conductors with either a signal and ground (un-balanced) or the same signal referenced to ground in both, but one is 180 degrees out of phase (balanced).



Other commonly seen transmission lines.

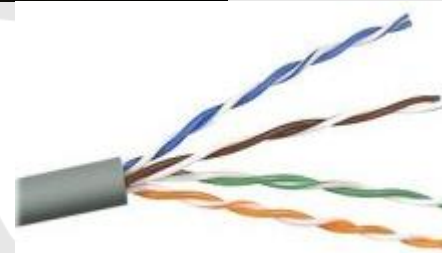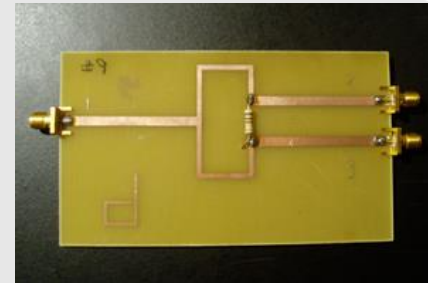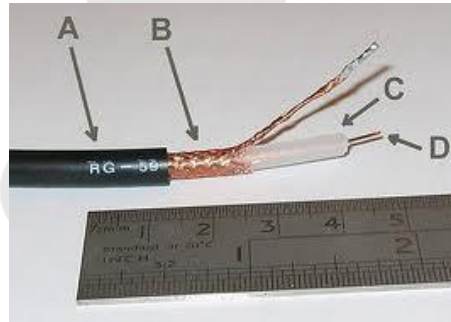
- Coaxial cable
 - TV and RF cables
- Stripline
- Microstrip
 - Cheaper and more widely used (PCB design)
- Twisted pair (balanced lines)
 - Widely used in everything from telephones to LANs



In transmission lines, size really does matter.

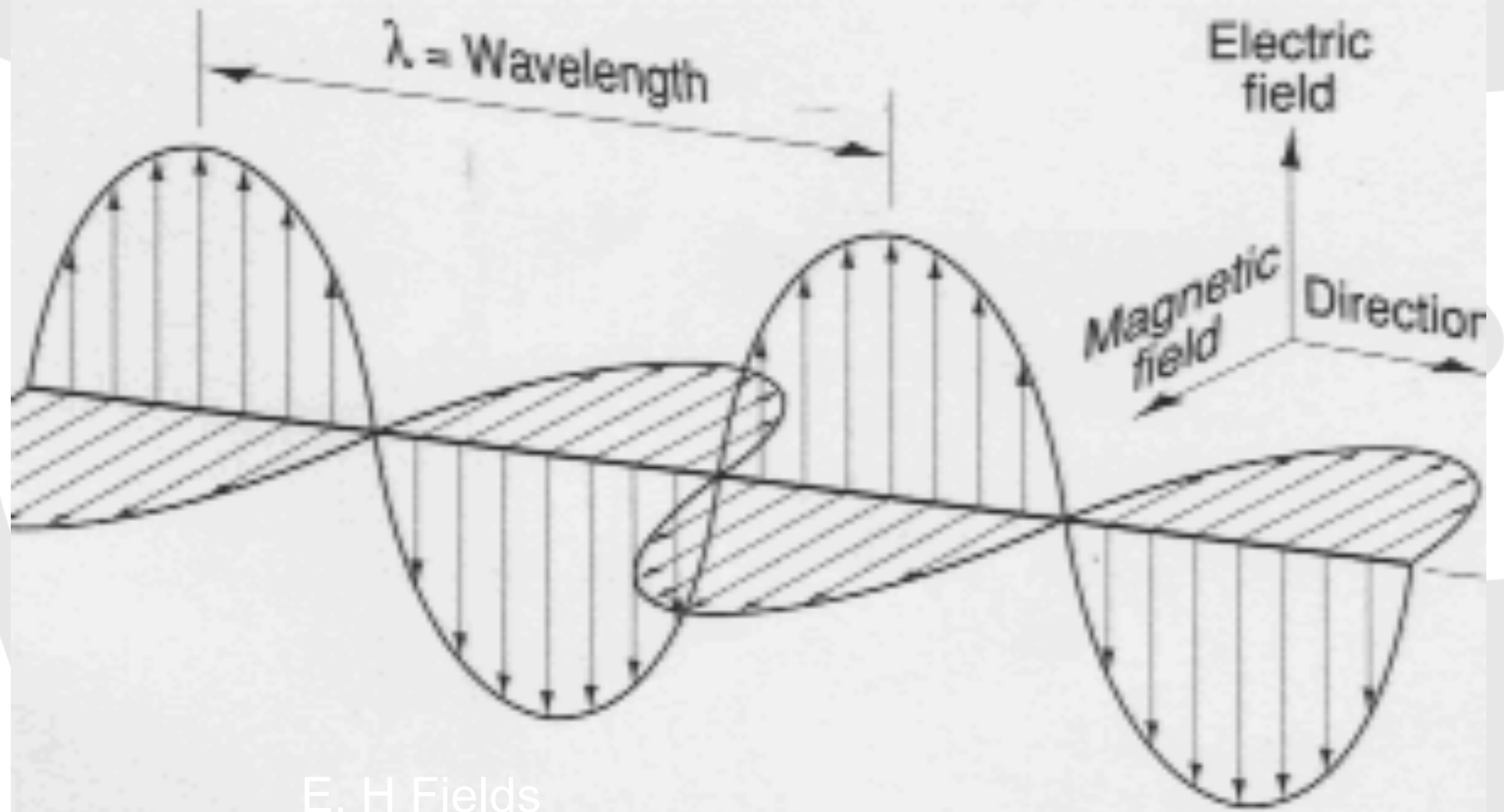- The length of the cable.
 - $>0.1\lambda$, one tenth of the wavelength of the transmitted signal.
- The frequency or wavelength of the transmitted signal.
 - Circuit theory is insufficient
- Ordinary cabling is not suitable for carrying these signals efficiently.
 - Reflection
 - Radiation
 - Equals losses






E, H Fields



UN
PL

E, H Fields for micro strip.

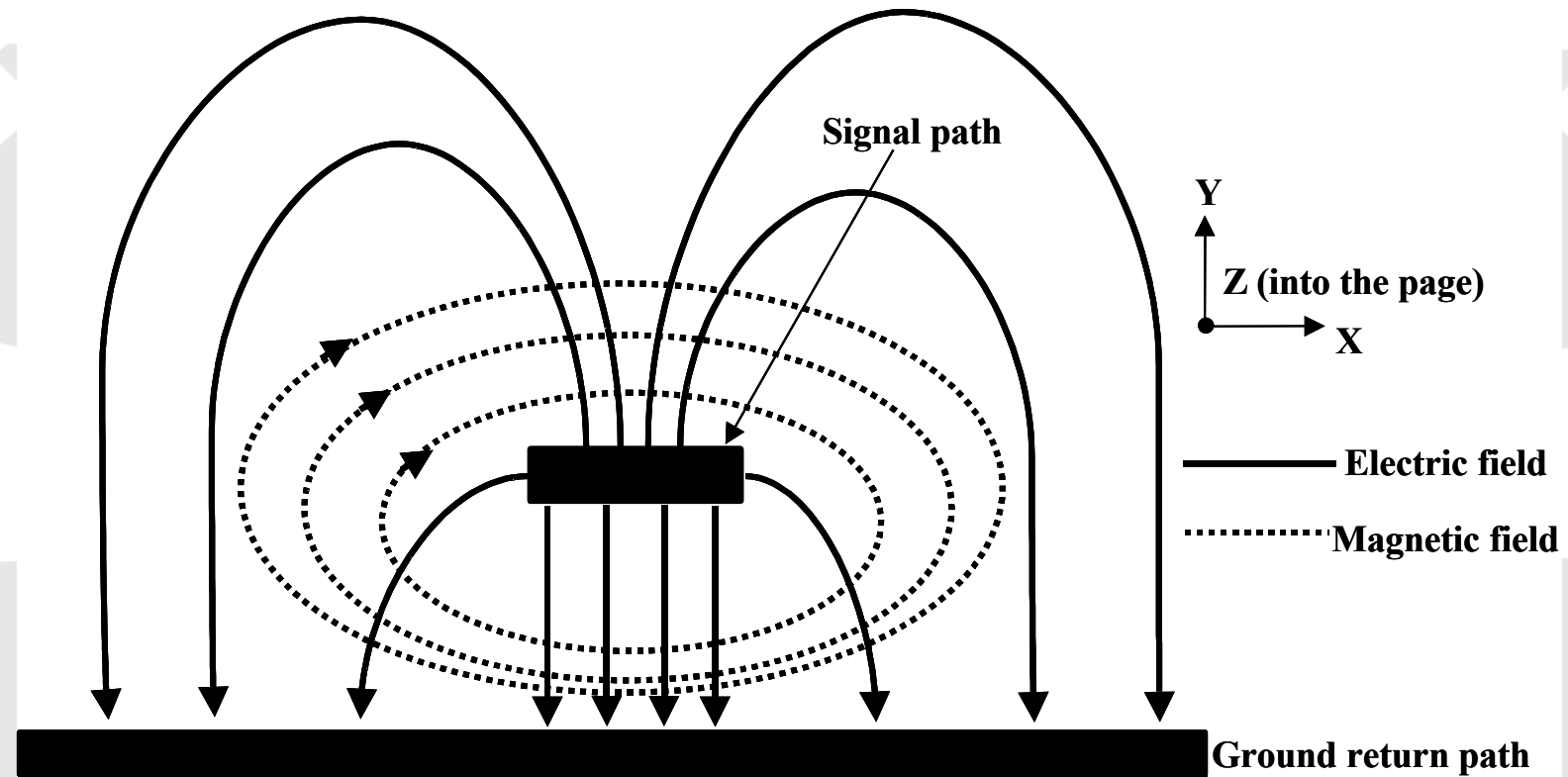

The signal is really the wave propagating between the conductors



UNIVERSITY OF
PLYMOUTH

A sense of scale

- The speed of light in free space is a top speed, but, in transmission lines and on copper this speed is considerably reduced.

- Free space, $c = 3000000000$ m/s


- Transmission line, $c = \sim 2400000000$ m/s

Frequency (GHz)	Wavelength λ (cm)	0.1λ (cm)
0.1	300	30
1	30	3
1.5	20	2
2	15	1.5
2.5	12	1.2
3	10	1
5	6	0.6
10	3	0.3
100	0.3	0.03




Characteristic impedance

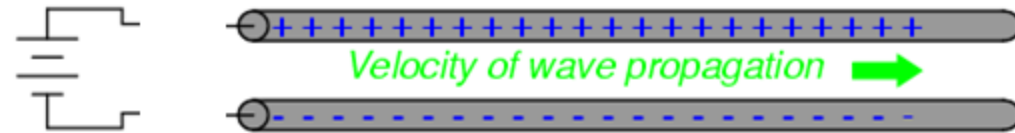- IMAGINE:
- A transmission line.
- Of infinite length
- With a battery disconnected.
- What happens when the battery is connected?



Transmission line models

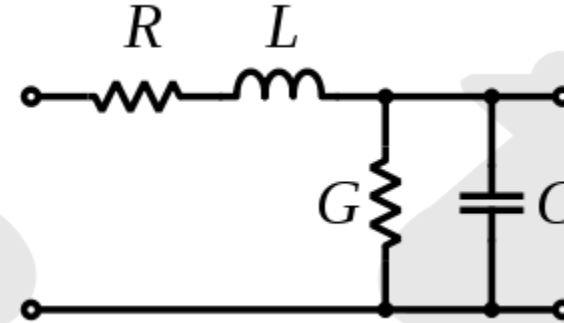Resistance (R), Inductance (L), Conductance (G), Capacitance (C), all per unit length.






Telegraphers Equations:

- Linear differential equations that allow the voltage and current to be found with respect to distance and time along a transmission line.
- A key expression is:

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

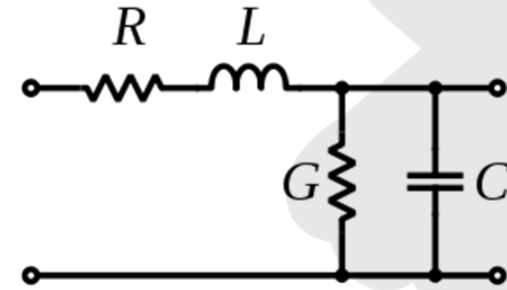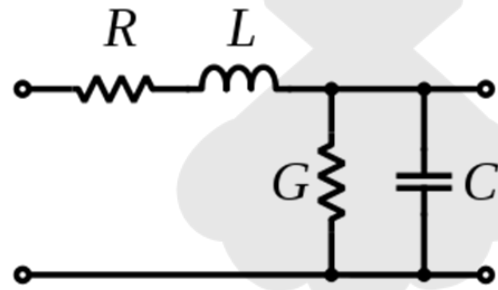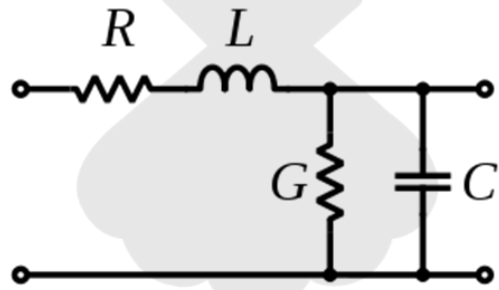- Which gives the Characteristic Impedance








Transmission line model



UNIVERSITY OF
PLYMOUTH


Transmission line models

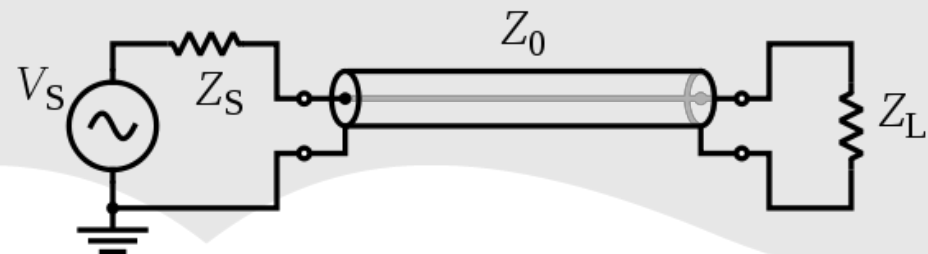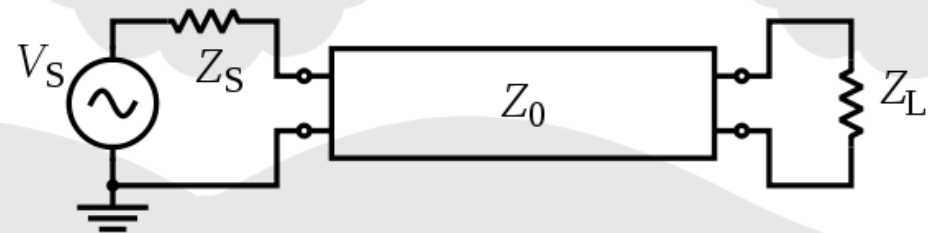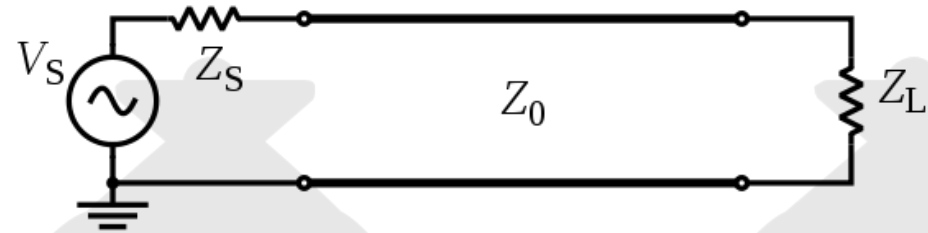- Where:
- Z_s = input impedance
- Z_0 = characteristic impedance
- Z_L = load impedance
- Special case:
 - The matched load



The universal serial bus (USB)

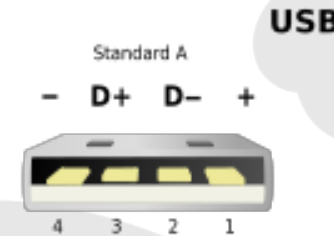- USB 1.1 (~1998)
- 1.5 Mbit/s Low speed (Max 3m)
- 12 Mbit/s Full speed (Max 5m)
- USB 2 (~2000)
- 480 Mbit/s High speed (Max 5m)
- USB 3 (~2010)
- 5 Gbit/s Super speed (Max ~??)
- How has this been achieved?



Twisted pair to reduce noise and crosstalk. Characteristic impedance of $\sim 90\Omega$



Serial advanced technology attachment (SATA)



A bus interface standard for connecting data storage devices like hard drives and optical drives to a host computer bus adaptor. Connects inside a PC

Pin	Function
1	Ground
2	A+ (transmit)
3	A- (transmit)
4	Ground
5	B- (receive)
6	B+ (receive)
7	Ground
-	Coding Notch

- Replaced parallel ATA and now provides data rates of 1.5, 3 and now 6 Gbit/s
- Allows longer cables, 1m compared to 40cm
- Smaller cables allow better airflow in chassis

Why change from parallel ATA (IDE).

- A better transmission line for the job
- Higher speed
- Better noise performance



Peripheral component interconnect express (PCIe)

- Replaces older bus standards
- PCI Express 1x250 [500]* MB/s
- PCI Express 2x500 [1000]* MB/s
- PCI Express 4x1000 [2000]* MB/s
- PCI Express 8x2000 [4000]* MB/s
- PCI Express 16x4000 [8000]* MB/s
- PCI Express 32x8000 [16000]* MB/s



Gigabit Ethernet

- Wired LAN standard.
 - How has it evolved?
 - Network protocols, packet size.
 - Cabling (The transmission lines)
- 1000BASE-T Twisted-pair cabling (Cat-5, Cat-5e, Cat-6, or Cat-7) 100 meters
- 1000BASE-TX Twisted-pair cabling (Cat-6, Cat-7) 100 meters

Pair	Wire	Color
3	tip	 white/green
3	ring	 green
2	tip	 white/orange
1	ring	 blue
1	tip	 white/blue
2	ring	 orange
4	tip	 white/brown
4	ring	 brown




Summary

Just a wire?

- Physical and electrical properties of transmission lines
 - Physical, the properties and design issues of cables.
 - Electrical, the circuit characteristics and equivalent models that are important in the specification and design of data transmission lines. How the physical properties relate to this.
 - The key theoretical and practical considerations in the use of transmission lines
- The properties and performance of a number of modern wired communication standards, USB, Gigabit Ethernet etc.
- How transmission lines are fundamental to their performance
- What happens next?



UNIVERSITY OF
PLYMOUTH

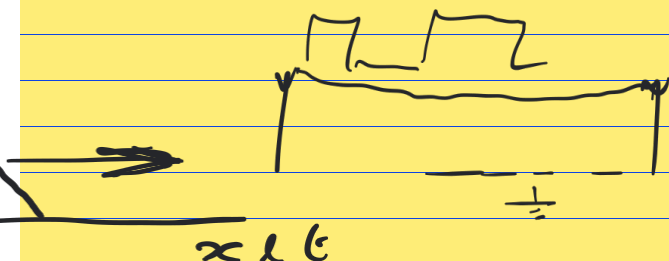

The Telegraphers equations.

Morse - 1837
Olive Heaviside - 1880

Ringings

Motherboard design & logic issue

Variation in voltage is related to distance, time & amb. vice versa for C amb.

A bit of maths to give us V or I in terms of distance & time + medium/structure.

$$\Delta V = -L \Delta x \frac{\partial I}{\partial t}$$

$$\Delta I = -C \Delta x \frac{\partial V}{\partial t}$$

how long does a pulse need to be to

settle.

ISI.

To much ringing = data loss

$$\frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t}$$

$$\frac{\partial I}{\partial x} = -C \frac{\partial V}{\partial t}$$

wrt x

$$\frac{\partial^2 V}{\partial x^2} = -L \frac{\partial^2 I}{\partial x \partial t}$$

$$\frac{\partial^2 I}{\partial x^2} = -C \frac{\partial^2 V}{\partial x \partial t}$$

wrt t

$$\frac{\partial^2 V}{\partial t \partial x} = -L \frac{\partial^2 I}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial t \partial x} = -C \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^4 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 V}{\partial x^2} - LC \frac{\partial^2 V}{\partial t^2} = 0$$

$$\frac{\partial^2 I}{\partial x^2} = LC \frac{\partial^2 I}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial x^2} - LC \frac{\partial^2 I}{\partial t^2} = 0$$

$$\frac{\partial^2 A}{\partial x^2} - \frac{1}{v_p^2} \frac{\partial^2 A}{\partial t^2} = 0$$

Wave Equation

General equation for any travelling wave. sound, light, etc

$$\frac{\partial^2 V}{\partial x^2} - LC \frac{\partial^2 V}{\partial t^2} = 0$$

$$\therefore \frac{1}{v_p^2} = LC$$

$$v_p = \frac{1}{\sqrt{LC}}$$

$$A_y = y = t - \frac{x}{v}$$

$$y = t + \frac{x}{v}$$



$$\begin{array}{cc} \rightarrow & \leftarrow \\ y = t - & y = t + \end{array}$$

General solution, both directions.

Like


$$V = V \sin \omega t.$$

$$V^+ = V(t - \frac{x}{v}) \quad \& \quad V^- = V(t + \frac{x}{v})$$

$$\frac{dV}{dt} = \dots \quad \frac{dV}{dx} = \dots$$

$$\frac{d^2V}{dt^2} = \dots \quad \frac{d^2V}{dx^2} = \dots$$

You can test this if you can!

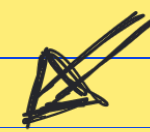

You will go down in history and be mentioned in future lectures for gals to come

V^+ & V^- are amplitudes


V^+ going left to right
 V^- going right to left

Putting in our solution

$$V(x,t) = V^+ \left(t - \frac{x}{v} \right) + V^- \left(t + \frac{x}{v} \right)$$

~~fwd~~ bwd
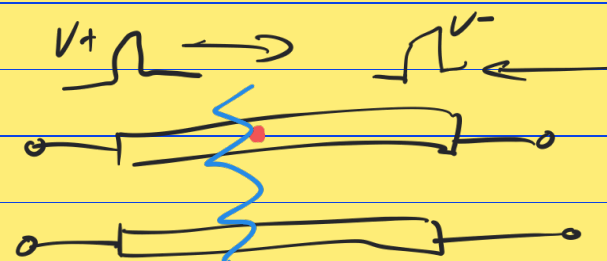
$$I(x,t) = \frac{V^+}{Z_0} \left(t - \frac{x}{v} \right) - \frac{V^-}{Z_0} \left(t + \frac{x}{v} \right)$$



Z_{in}

look at this pt on the line



$$R = Z_{in} = \frac{V}{I} = Z_0 \frac{(V^+ + V^-)}{(V^+ - V^-)}$$

$$Z_0 = 75 \Omega \text{ vs } 50 \Omega ??$$

$$Z_{in} = Z_L = \frac{V}{I} = Z_0 \frac{(V^+ + V^-)}{(V^+ - V^-)}$$

$$\Rightarrow \frac{V^-}{V^+} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\Rightarrow \Gamma \quad (\text{Greek Gamma})$$

Voltage reflection coeff

$$\text{Matched line} = \frac{50 - 50}{50 + 50} = 0$$

$$|\Gamma| \leq 1$$

$$-\Gamma = \frac{I^-}{I^+}$$

Current reflection coeff.

REFLECTION COEFFICIENT

$$\Gamma = \frac{V^-}{V^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Current " " = $-\Gamma$

V^+ & V^- are amplitudes


V^+ going left to right
 V^- going right to left

Putting in our solution

$$V(x,t) = V^+ \left(t - \frac{x}{v} \right) + V^- \left(t + \frac{x}{v} \right)$$

~~fwd~~ bwd
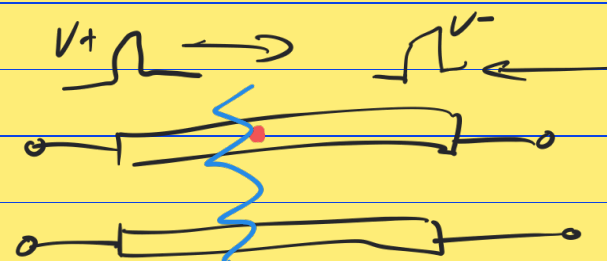
$$I(x,t) = \frac{V^+}{Z_0} \left(t - \frac{x}{v} \right) - \frac{V^-}{Z_0} \left(t + \frac{x}{v} \right)$$



Z_{in}

look at this pt on the line



$$R = Z_{in} = \frac{V}{I} = Z_0 \frac{(V^+ + V^-)}{(V^+ - V^-)}$$

$Z_0 = 75 \Omega$ vs 50Ω ??

$$Z_{in} = Z_L = \frac{V}{I} = Z_0 \frac{(V^+ + V^-)}{(V^+ - V^-)} \Rightarrow \frac{V^-}{V^+} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

Γ (Greek Gamma)
 Voltage reflection coeff

$$\text{Matched line} = \frac{50 - 50}{50 + 50} = 0$$

$$|\Gamma| \leq 1$$

$$-\Gamma = \frac{I^-}{I^+}$$

Current reflection coeff.

REFLECTION COEFFICIENT

$$\Gamma = \frac{V^-}{V^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Current " " = $-\Gamma$

$$\Gamma = \text{reflection coefficient} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

Symmetrical so $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$



What is the reflection coefficient $\Gamma =$
 How much gets reflected? $=$

look at the animation on wikipedia
 but note, this is for a load less than Z_0 as it reflects/returns on the ground.

Home work ☺

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \quad -\Gamma = ?$$

① Why is $Z_0 = 50\Omega$ chosen for RF applications & 75Ω for terrestrial TV? (Google it)


② What is the reflection coefficient Γ for an open circuit.

③ " short circuit

④ " matched load

$$\text{so } Z_0 = Z_L = 50\Omega$$

$$V_{SWR} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

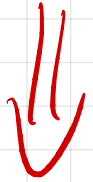

Find the range of
values. Homework

$$\text{Return loss} = R_{L\text{dB}} = 10 \log \frac{P_r}{P_i}$$

Also

$$= -20 \log |\Gamma|^2$$


$$\text{Power} = V \cdot I$$

$$I = \frac{V}{R}$$

$$= V \cdot \frac{V}{R}$$

$$P = V^2$$

Example

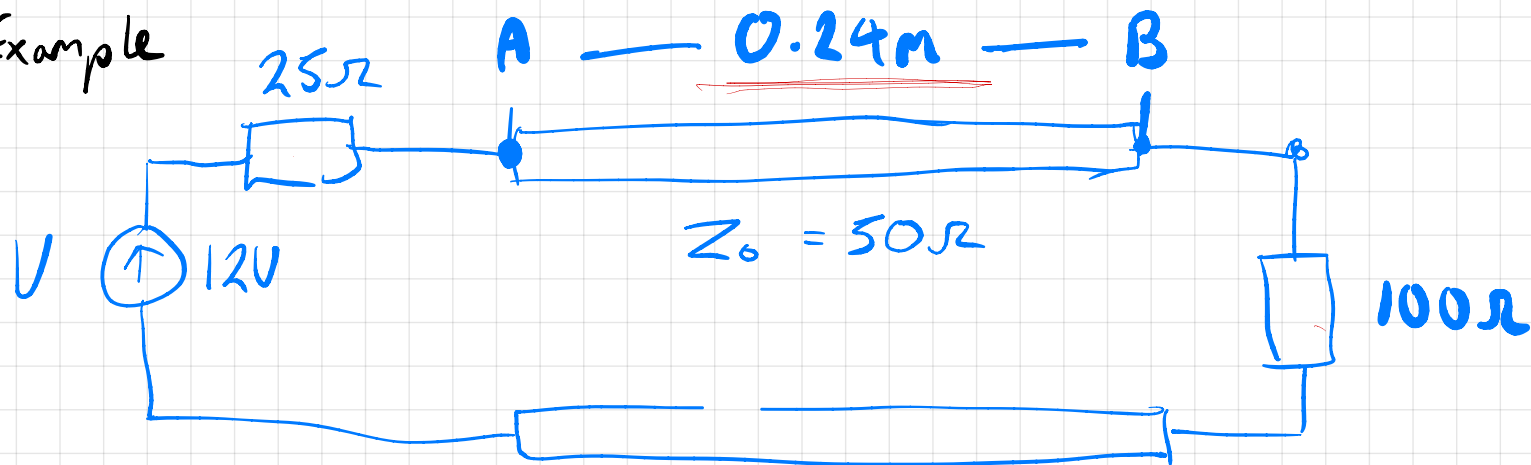

$$V_p = 2.4 \times 10^8 \text{ m/s}$$

How much voltage goes onto the line at the start

