

Electrical and Electronics Engineering and Robotics

ELEC345 High Speed Communications

Double stub matching

Dr Toby Whitley



UNIVERSITY OF
PLYMOUTH




Remember - Single stub Match.

$$Z_0 = 50\Omega$$

$$Z_L = 30 + 25j$$

$$Z = 0.6 + 0.5j$$

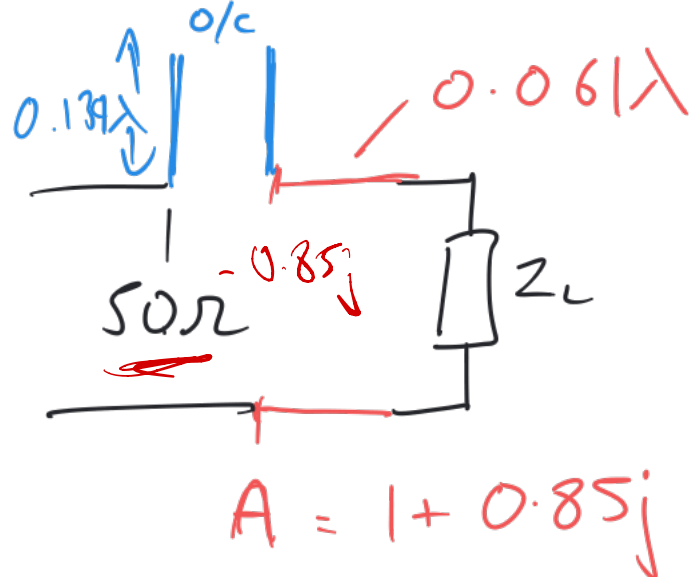


Stub must equal $-0.85j$


$$\begin{aligned} \text{o/c stub } 0.389\lambda - 0.25\lambda \\ = 0.139\lambda \end{aligned} \quad \text{s/c} = -0.85j$$

- ① Rotate bwd gen round VSWR circle until you hit matching circle. Real of dist 0.061λ
- ② Look at how much j needs adding or removing. ($-0.85j$)
- ③ Choose type & find length of stub needed to give this
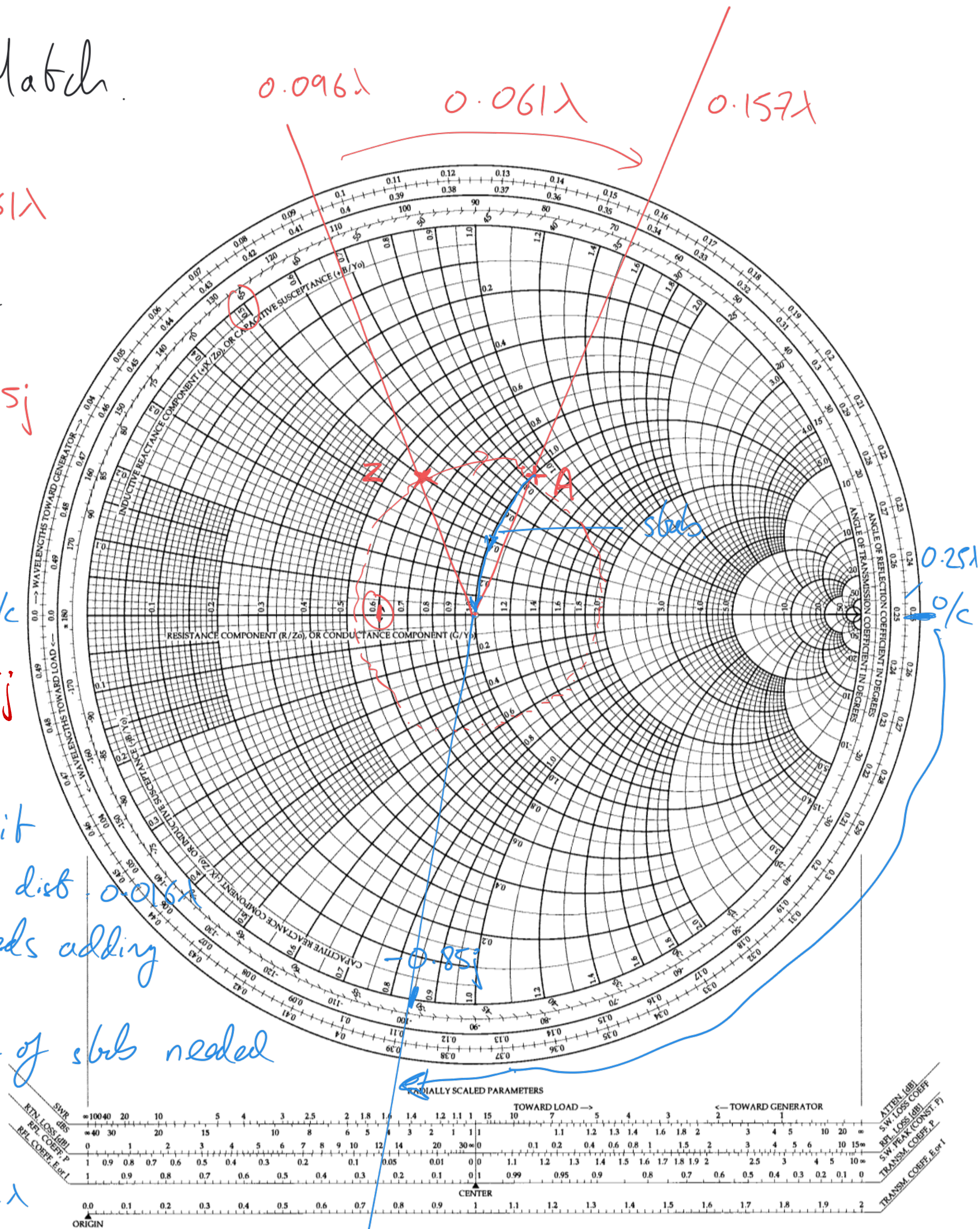
$$\begin{aligned} \text{o/c. bwd gen} \\ \text{from } 0.25\lambda \rightarrow 0.389\lambda \\ = 0.139\lambda \end{aligned}$$


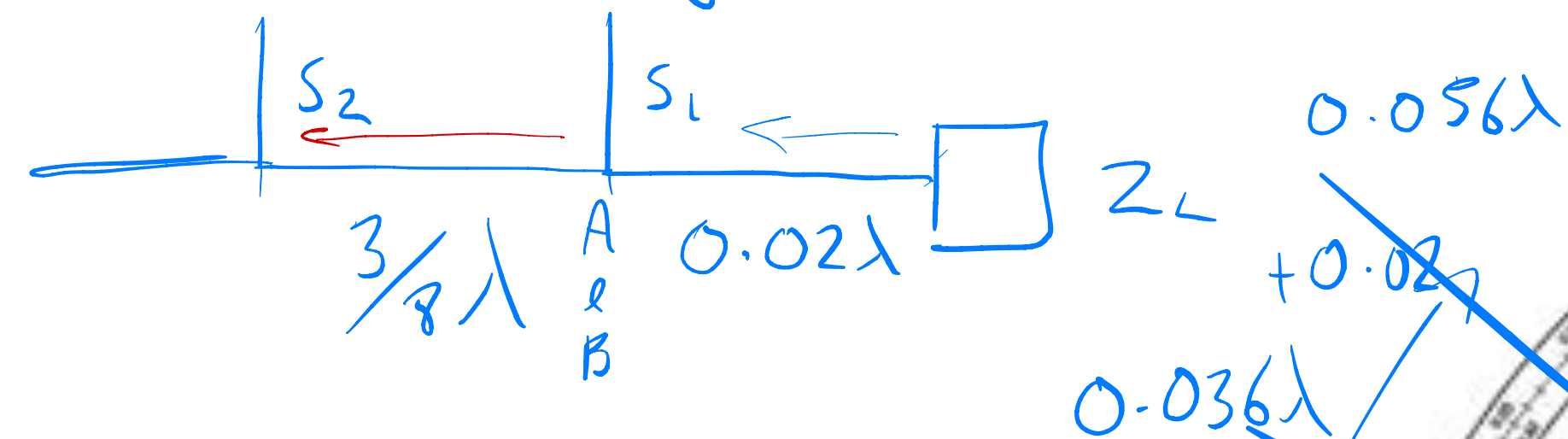
$$Z_L = 20 + 10j \quad \text{Normalize } (\div 50) \Rightarrow 0.4 + 0.2j$$



To A is $0.3j \rightarrow -0.15j = -0.45j$


T B is $0.3j \rightarrow -1.9j = -2.2j$
use o/c stub for entire $\uparrow$ s/c.

$$A' = 1 - 0.9j \quad B' = 1 + 2.9j$$

Lastly 2nd stub removes $\pm j$ from A' & B'

$1 + 2.2j$ so o/c stub for $-2.2j$

$1 - 0.9$ so use s/c stub $+0.9j$

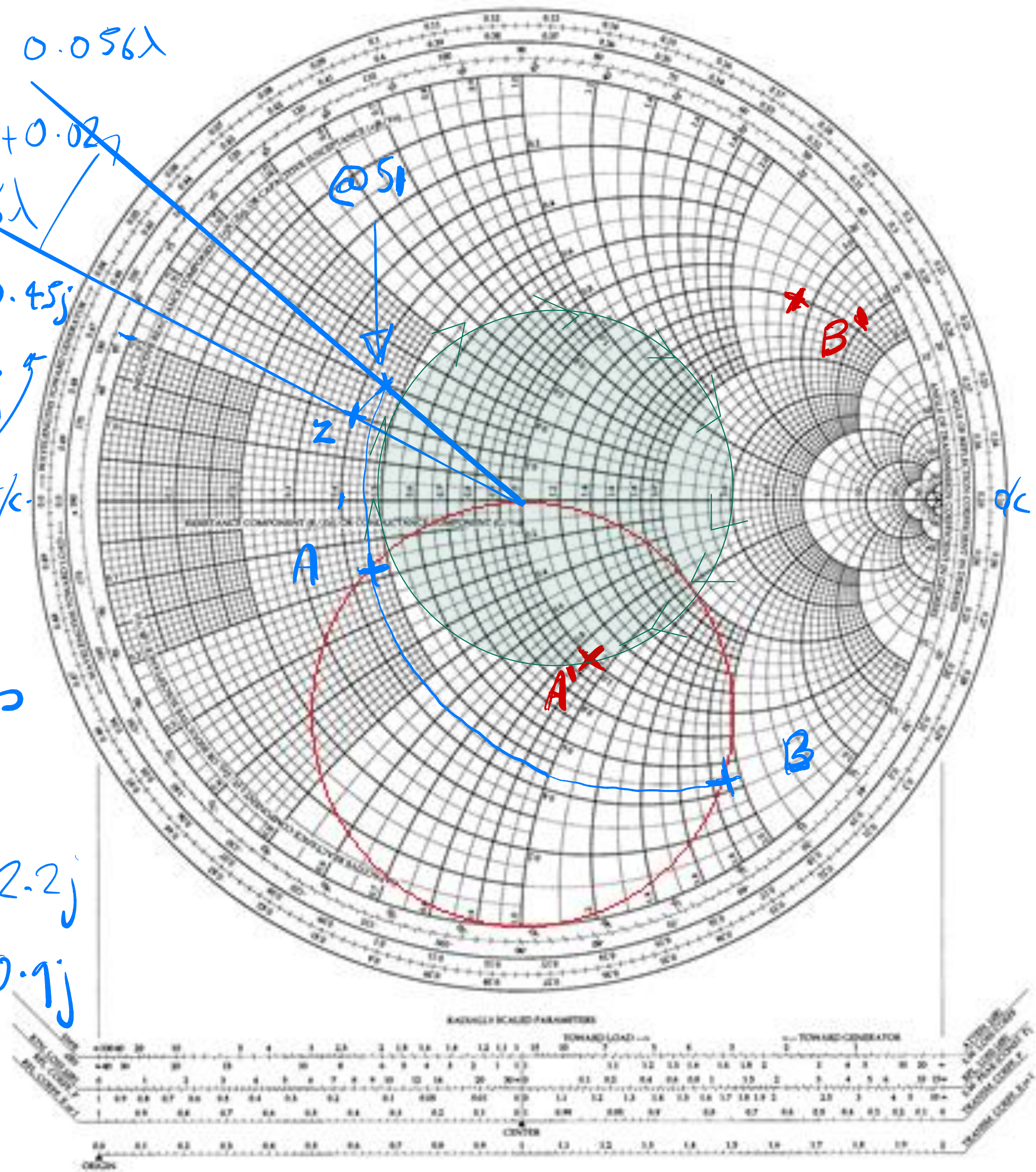

Parallel Double stub matching steps

- ① Plot load. $Y_L \times 50$ $Z_L \div 50$ then transpose to Y_L
- ② Rotate to the first stub s_1 often 0.02λ but can be a choice
- ③ Use stub 1 to add or subtract j onto $3/8\lambda$ guide circle
- ④ Calculate length of stub for this j
- ⑤ Rotate $3/8\lambda$ to stub 2 and onto matching circle.
- ⑥ Use stub 2 to add or subtract j to centre
- ⑦ Calculate length of stub 2 for required j .

Remember to transpose s/k & o/c for parallel matching

